

Attempt any three questions -

Q. 1. Explain the following -

- (i) Resonance frequency
- (ii) Bandwidth
- (iii) Q-factor
- (iv) selectivity

Q. 2. In a series R-L-C circuit, $R = 10 \Omega$, $L = 0.1 \text{ H}$, $C = 8 \mu\text{F}$
calculate - (i) Resonance frequency (ii) Q-factor
(iii) Half power frequencies (iv) Bandwidth

Q. 3. Find Laplace Transform of $\cos(\omega t + \theta)$

Q. 4. Find Inverse Laplace Transform of $F(s) = \frac{1}{s(s^2 + 4s + 4)}$

Ans. 1. (i) In a series R-L-C ckt.

at resonance $X_L = X_C$, $\omega L = \frac{1}{\omega C}$

$$\omega^2 = \frac{1}{LC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad 2\pi f_0 = \frac{1}{\sqrt{LC}}, \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

f_0 is resonance frequency at which resonance occurs.

(ii) Frequencies at which current is $\frac{1}{\sqrt{2}}$ times of the max^m current at resonance are called half power frequencies f_1 & f_2

$$f_2 - f_1 = \text{B.W.} = \frac{R}{2\pi L}$$

(iii) Q-factor is defined as voltage magnification at resonance

$$\text{Q-factor} = \frac{\text{voltage drop across L or C at resonance}}{\text{Supply voltage at resonance}}$$

$$= \frac{I_0 X_L}{I_0 R} = \frac{X_L}{R} = \frac{\omega_0 L}{R}$$

$$= 2\pi f_0 \frac{L}{R} = 2\pi \cdot \frac{L}{R} \cdot \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{or Q-factor} = 2\pi \times \frac{\text{Maximum energy stored}}{\text{energy dissipated per cycle}}$$

(iv) Selectivity - It indicates the ability of a circuit to select a particular bandwidth. It is the ratio of the bandwidth to the resonant frequency. Thus

$$\text{Selectivity} = \frac{f_2 - f_1}{f_0} = \frac{\text{B.W.}}{f_0}$$

Ans. 2. $R = 10 \Omega$, $L = 0.1 H$, $C = 8 \mu F$

$$(i) f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 8 \times 10^{-6}}} = 178 \text{ Hz}$$

$$(ii) Q\text{-factor} = \frac{1}{R}\sqrt{\frac{L}{C}} = \frac{1}{10}\sqrt{\frac{0.1}{8 \times 10^{-6}}} = 11.18$$

$$(iii) f_1 = f_0 - \frac{R}{4\pi L} = 178 - \frac{10}{4\pi \times 0.1} = 170 \text{ Hz.}$$

$$f_2 = f_0 + \frac{R}{4\pi L} = 178 + \frac{10}{4\pi \times 0.1} = 186 \text{ Hz}$$

$$(iv) \text{B.W.} = f_2 - f_1 = 186 - 170 = 16 \text{ Hz}$$

Ans. 3. $f(t) = \cos(\omega t + \theta)$

$$F(s) = L[\cos(\omega t + \theta)]$$

$$= L[\cos \omega t \cos \theta - \sin \omega t \sin \theta]$$

$$= L[\cos \omega t \cos \theta] - L[\sin \omega t \sin \theta]$$

$$= \cos \theta L[\cos \omega t] - \sin \theta L[\sin \omega t]$$

$$= \cos \theta \cdot \frac{s}{s^2 + \omega^2} - \sin \theta \cdot \frac{\omega}{s^2 + \omega^2}$$

$$= \frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$$

Ans. 4. $F(s) = \frac{1}{s(s^2+4s+4)}$

$$\frac{1}{s(s^2+4s+4)} = \frac{1}{s(s+2)^2} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

$$\frac{1}{s(s+2)^2} = \frac{A(s+2)^2 + Bs(s+2) + Cs}{s(s+2)^2}$$

$$1 = A(s+2)^2 + Bs(s+2) + Cs$$

$$1 = A(s^2+4s+4) + B(s^2+2s) + Cs$$

$$1 = s^2(A+B) + s(4A+2B+C) + 4A$$

comparing coefficients of s^2 , s & constant

$$4A = 1, \quad A = \frac{1}{4}$$

$$A+B=0 \quad B=-A = -\frac{1}{4}$$

$$4A+2B+C=0$$

$$4\left(\frac{1}{4}\right) + 2\left(-\frac{1}{4}\right) + C = 0$$

$$1 - \frac{1}{2} + C = 0$$

$$\frac{1}{2} + C = 0 \quad C = -\frac{1}{2}$$

Putting values of A , B & C

$$F(s) = \frac{1}{s(s+2)^2} = \frac{1}{4s} - \frac{1}{4} \cdot \frac{1}{s+2} - \frac{1}{2} \cdot \frac{1}{(s+2)^2}$$

Taking Inverse Laplace Transform

$$L^{-1}[F(s)] = L^{-1}\left[\frac{1}{4s} - \frac{1}{4(s+2)} - \frac{1}{2(s+2)^2}\right]$$

$$= L^{-1}\left[\frac{1}{4s}\right] - L^{-1}\left[\frac{1}{4(s+2)}\right] - L^{-1}\left[\frac{1}{2(s+2)^2}\right]$$

$$= \frac{1}{4}L^{-1}\left[\frac{1}{s}\right] - \frac{1}{4}L^{-1}\left[\frac{1}{s+2}\right] - \frac{1}{2}L^{-1}\left[\frac{1}{(s+2)^2}\right]$$

$$f(t) = \frac{1}{4} - \frac{1}{4}e^{-2t} - \frac{1}{2}te^{-2t}$$