

EE205. Digital Electronics

IInd Test 17/1/18

Q.1 Reduce the following Boolean expression.

(a) $A + \bar{A}B + AB$

(b) $A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$

Ans.

(a)

$$A + \bar{A}B + AB$$

$$A + B(\bar{A} + A)$$

$$A + B \cdot 1 \quad | \because \bar{A} + A = 1$$

$$A + B$$

(b) $A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$

$$A\bar{B} + AB + \bar{A}B + \bar{A}\bar{B}$$

$$A(\bar{B} + B) + (B + \bar{B})\bar{A}$$

$$(A + \bar{A})(B + \bar{B})$$

$$1 \cdot 1$$


$$\Rightarrow 1.$$

$$\because \bar{A} + A = 1$$

$$\therefore \bar{B} + B = 1$$

Q.2 Explain all logic gates.

Ans. Symbols of logic gates

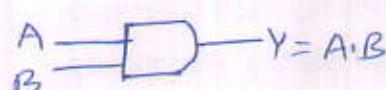

(i) $Y = A \cdot B$
AND gate



(ii) OR gate



(iii) NOT gate

Truth table

AND gate


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


NOT gate

A	Y
0	1
1	0

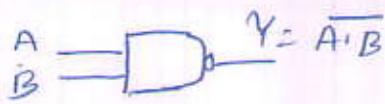


NAND gate

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

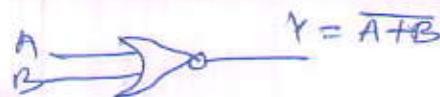

NOR gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

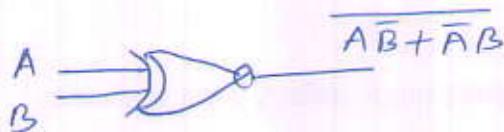

Ex-NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1



Ex-OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Q3 Explain DeMorgan's theorem.

Ans : i) DeMorgan's 1st theorem

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

NOR gate = Bubbled AND gate
input

ii) DeMorgan's 2nd theorem

$$\overline{AB} = \overline{A} + \overline{B}$$

NAND gate = Bubbled OR gate
input

Q.4 Solve the function using k-map?

$$\Sigma m(0, 2, 5, 7, 8, 10, 12, 15)$$

Ans.

$$Y = \Sigma m(0, 2, 5, 7, 8, 10, 13, 15)$$

Step I This is 4 variables Boolean function. So we ~~have~~ draw the 4 variable K-map.

Step II Draw 4 variable Kmap and fill it with given minterms

		CD					
		00	01	11	10		
AB	00	1			1		
	01		1	1	1		1
AB	11	1	1	1	1		1
	10	1	1	1	1	1	1

G_1 (quad) G_2 (quad)

$$Y = G_1 + G_2$$

$$= BD + \bar{B}\bar{D}$$

Q.5 Write down standard SOP form for

$$Y = \bar{A}B + \bar{A}\bar{B}C + \bar{A}C$$

Ans. $Y = \bar{A}B + \bar{A}\bar{B}C + \bar{A}C$

$$Y = \bar{A}B(C + \bar{C}) + \bar{A}\bar{B}C + \bar{A}C(B + \bar{B})$$

$$\Rightarrow \bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C$$