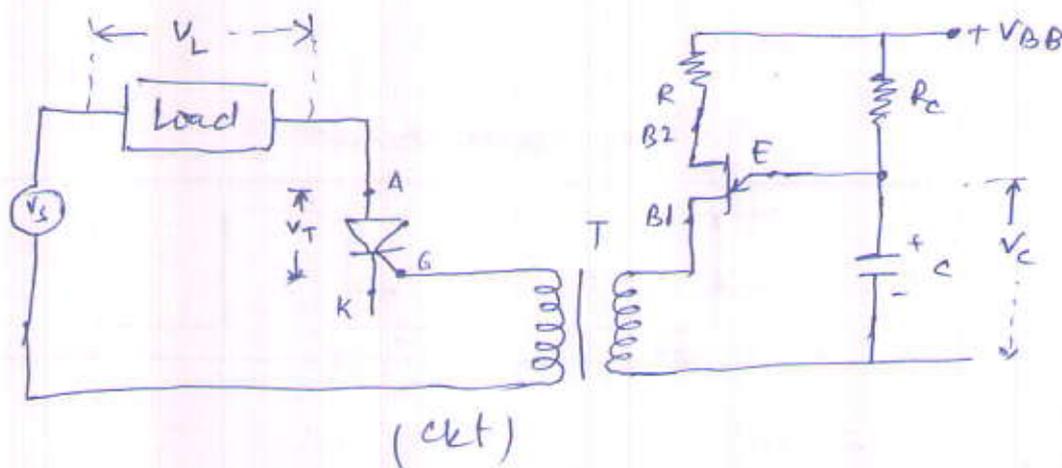


Ques. 1 Explain Phase control of SCR using UJT ckt. (5)




① The exact point of firing of SCR depends on appearance of gate pulse.

② Appearance of gate pulse depends the firing of UJT

③ The UJT is used here as a relaxation oscillator to obtain sharp repetitive pulses.

④ The pulse transformer is used to isolate the control ckt from main circuit

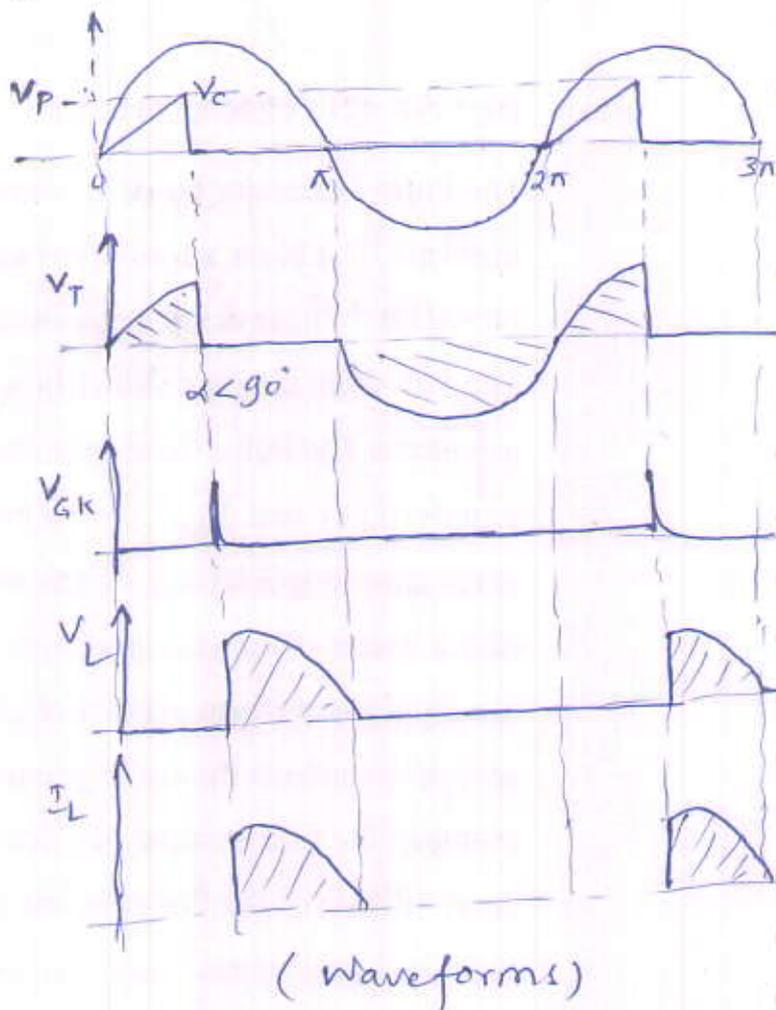⑤ The UJT breaks down when the voltage between



emitter and base B1 reaches the peak voltage V_p given by equation:

$$V_p = \eta V_{BB} + V_D$$

where η = intrinsic stand of ratio

V_D = diode cut in voltage

V_{BB} = Applied voltage to UJT, R_c and Cap.

⑥ Initially capacitor starts charging from 0V to reach maximum voltage V_p . At V_p , UJT fires, and capacitor discharges through emitter and a pulse occurs to trigger in thyristor.

⑦ The cap. voltage V_c depends on time constant R_c

$$T = R_c \cdot C$$



where T = time const of ckt

⑧ As soon as the pulse in the primary of the pulse transformer appears, a pulse at the secondary of the transformer also appears and UJT fires.


⑨ Before firing of SCR, the whole input voltage appears across thyristor as V_T . After firing of SCR, the whole input voltage appears across the load as V_L .

⑩ The V_L and I_L waveforms are same b'coz the load is resistive.

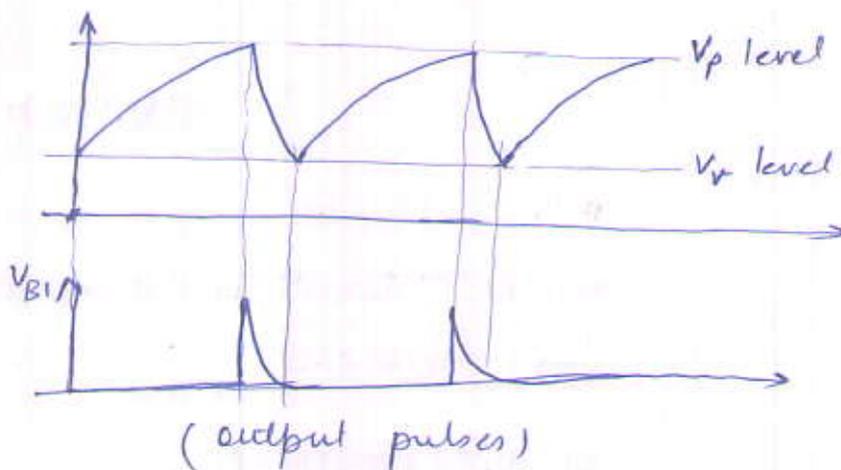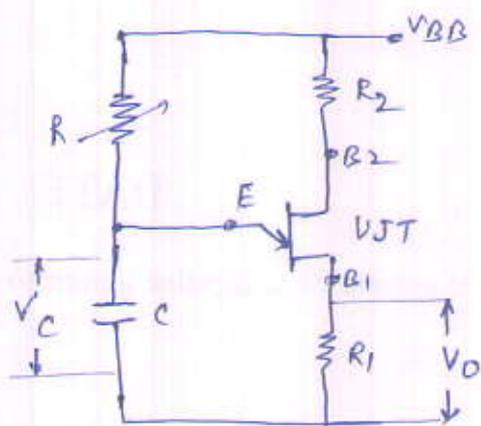Ques 2 Explain UJT as a relaxation Oscillator circuit,



- ① Since the UJT exhibit the negative resistance characteristic it can be used as relaxation oscillator as shown above
- ② the external resistances R_1 and R_2 in comparison with the internal resistances R_{B1} and R_{B2} of UJT base
- ③ the charging resistance R should be such that its load line intersect the device characteristic only in negative resistance region
- ④ As the power supply is switched on, the cap. C starts charging to the supply voltage V_{BB} through resistance R

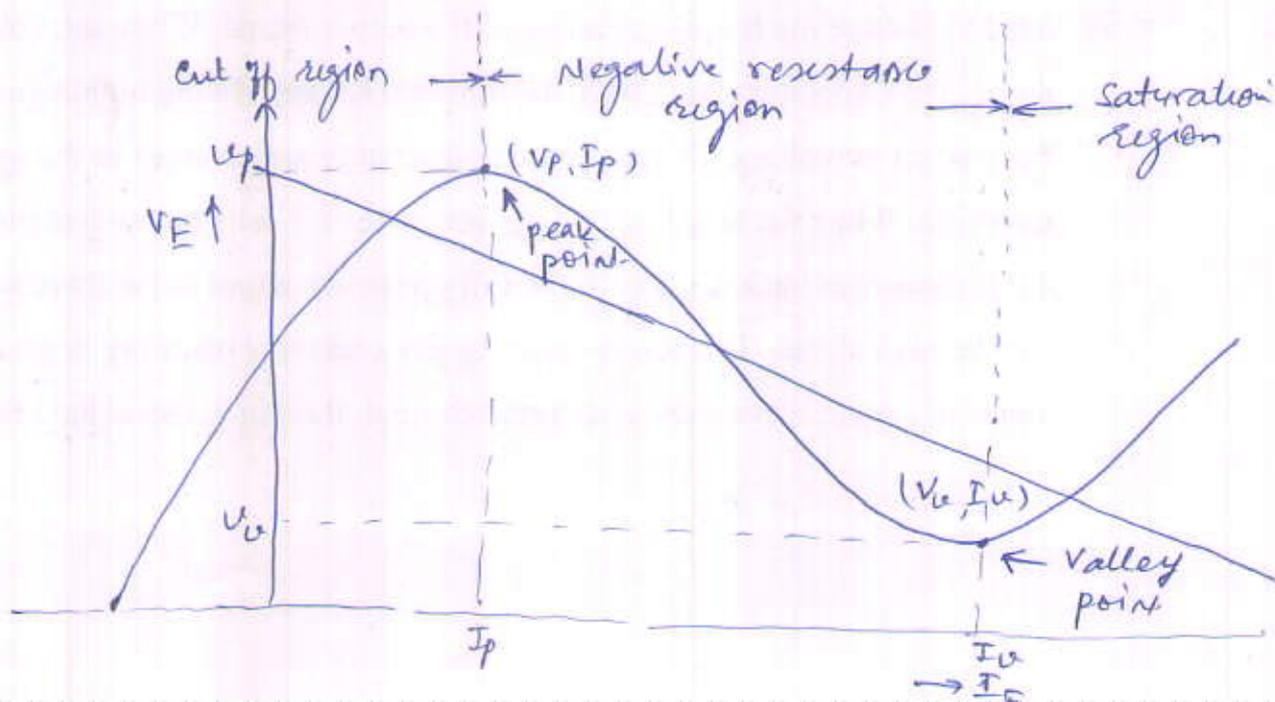

The capacitor charges with a time const $R_c \cdot C$ or R_c

- ⑤ When $V_c < V_p$, the UJT is off
- ⑥ As time passes, the V_c becomes equal to V_p and the UJT fires. and the capacitor starts discharging through R_1 and a pulse obtained across R_1
- ⑦ The voltage across cap during charging is

$$V_c = V_{BB} (1 - e^{-\frac{t}{R_c C}}) \quad \text{--- ①}$$

The voltage level at which UJT fires is $V_c = V_p = \eta V_{BB}$ --- ②

From ① and ②

$$V_{BB} (1 - e^{-\frac{t}{R_c C}}) = \eta V_{BB}$$

$$1 - e^{-\frac{t}{R_c C}} = \eta$$

$$1 - \eta = e^{-\frac{t}{R_c C}}$$

Taking log to both sides

$$\ln(1 - \eta) = -\frac{t}{R_c C}$$

$$\Rightarrow \frac{t}{R_c C} = \ln\left(\frac{1}{1 - \eta}\right)$$

$$\Rightarrow \frac{1}{f} = \frac{1}{R_c C \ln\left(\frac{1}{1 - \eta}\right)}$$



$$f = \frac{1}{R_c C \ln\left(\frac{1}{1 - \eta}\right)}$$

$$f = \frac{1}{2.303 R_c C \log\left(\frac{1}{1 - \eta}\right)}$$

where η = intrinsic stand off ratio


Ans 3

Write short Note on DIAC

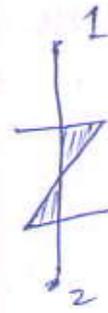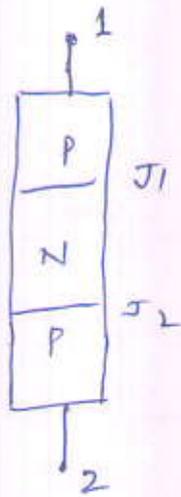

(schematic representation and symbol)

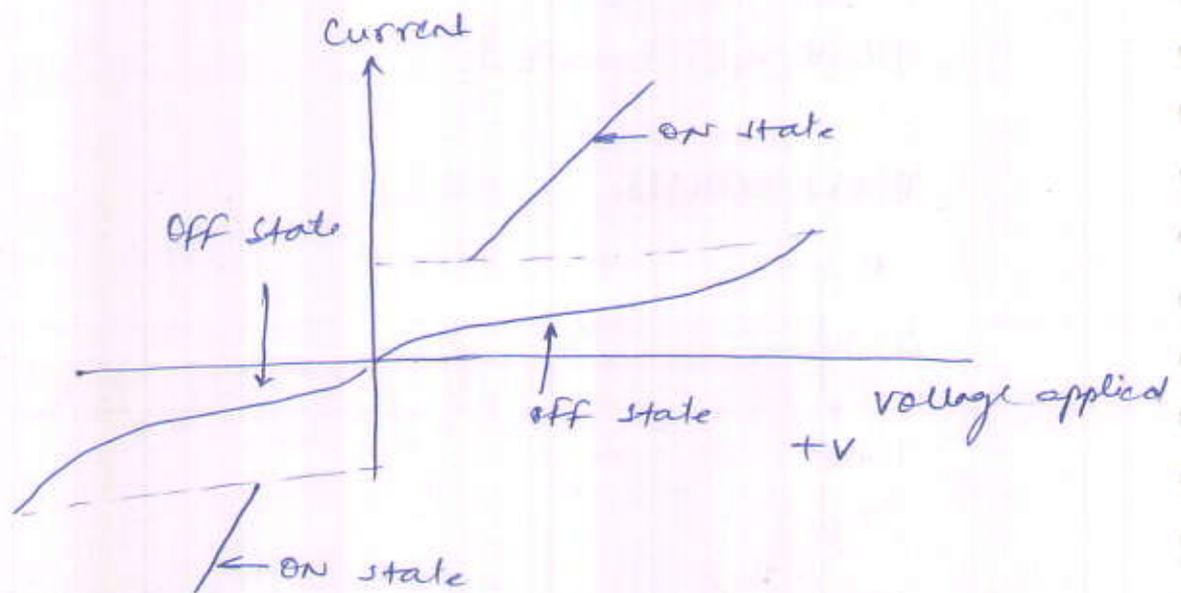- ① DIAC is a two electrode, three layer bidirectional avalanche diode which can be switched from OFF to ON state for either polarity of applied voltage.



- ② No gate terminal
- ③ Switching from off to on state is achieved by exceeding avalanche breakdown voltage in either direction
- ④ Two p-regions should have similar doping character resulting in symmetrical characteristic for both positive and negative voltages.

⑤ When voltage is applied, small saturation current appears across reverse biased P-N Jn.

⑥ When $V_{\text{applied}} > V_{\text{avalanche}}$,

the diac current increases sharply

and DIAC becomes turn on. In this turn on state, the voltage across the diac decreases sharply with increasing current

⑦ DIAC is a diode which works on AC

⑧ DIAC is mainly used for triggering of TRIAC

⑨ DIAC breakdown voltage is 30V. While conducting, it acts like a low resistance with 3V drop across it