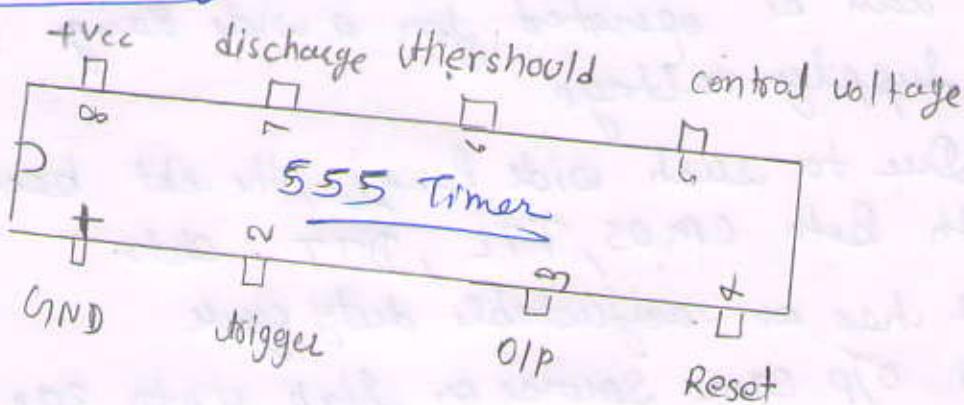


EL- 307


II Test (Linear Integrated Circuits  
and Design)  
18/11/18

(a) Write Short Note on I.C 555 Timer.

(a) PIN Diag.



(b) Block Diagram of 555 Timer

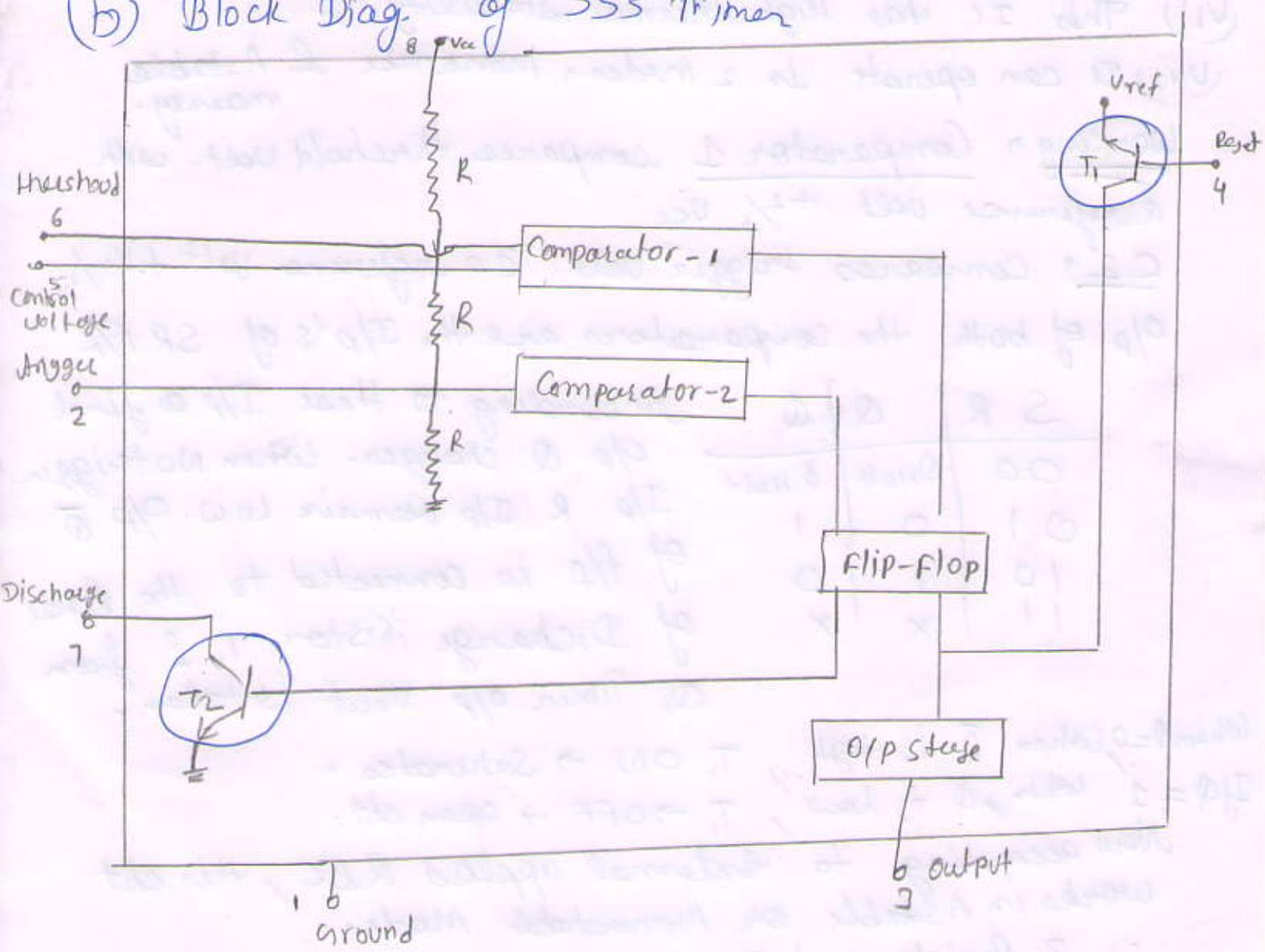

IC 555 is a most popular IC having features.

- ① It can produce accurate time delays of time periods ranging from microseconds to several hrs.
- ② It can be operated for a wide range (+5 to +15V) of supply voltage.
- ③ Due to such wide range, the circuit becomes compatible with both CMOS, TTL, DTL circuits.
- ④ It has an adjustable duty cycle.
- ⑤ Its O/P can source or sink upto 200 mA
- ⑥ It has a high current O/P.
- ⑦ This IC has high thermal stability.
- ⑧ It can operate in 2 modes, Monostable & Astable mainly.

Working  $\rightarrow$  Comparator 1 compares threshold volt. with a reference volt.  $+2/3 V_{cc}$

Comparator 2 compares trigger volt. with a reference volt.  $+V_{cc}/3$ .  
O/P of both the comparators are the I/P's of SR F/F.

S R	Q	$\bar{Q}$
00	Q <sub>Hold</sub>	$\bar{Q}_{Hold}$
01	0	1
10	1	0
11	X	X

According to these I/P's Q final  
 $\bar{Q}$  changes. When NOT triggered  
I/R R I/P Remains Low. O/P  $\bar{Q}$   
of f/f is connected to the base  
of Dischargeistor T<sub>1</sub> & from  
Q, Timer O/P V<sub>out</sub> is taken.


When  $\bar{Q}=0$ , when  $\bar{Q}$  is High, T<sub>1</sub> ON  $\rightarrow$  saturates.  
If  $\bar{Q}=1$  when  $\bar{Q}$  is low, T<sub>1</sub> OFF  $\rightarrow$  open ckt.

Now according to external applied RLC, this circuit works in Astable or Monostable Mode.

- 3 Resistors of 5kΩ are connected in series, so it's called 555 Timer.

Q(2) Explain the working of Adder & Subtractor using op-amp.

### Adder

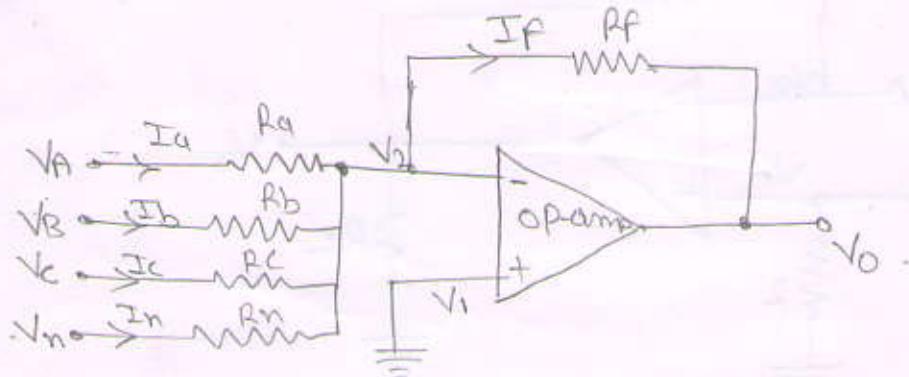

OP-AMP का Input Resistance तथा Voltage में से कोने पर

$$I_a + I_b + I_c + \dots + I_n = I_f$$

Apply KCL at Node V2

$$I_a + I_b + I_c = I_f + I_B$$

$$I_a + I_b + I_c = I_f$$

$$\frac{V_a - V_2}{R_a} + \frac{V_b - V_2}{R_b} + \frac{V_c - V_2}{R_c} = \frac{V_2 - V_o}{R_f} \quad \text{--- (3)}$$

high input impedance. Approximate

$$I_B \approx 0$$

$$V_1 = V_2 = 0$$

$$V_2 \approx 0$$

From (3)

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$


$$R_a = R_b = R_c = R_{in}$$

$$= \frac{1}{R_{in}} (V_a + V_b + V_c)$$

If  $R_f = R_a = R_b = R_c$  then O/P Vol =  $\frac{-1}{R_{in}}$  sum of I/P Voltage

$$\text{then } V_o = -(V_a + V_b + V_c)$$

## Subtractor

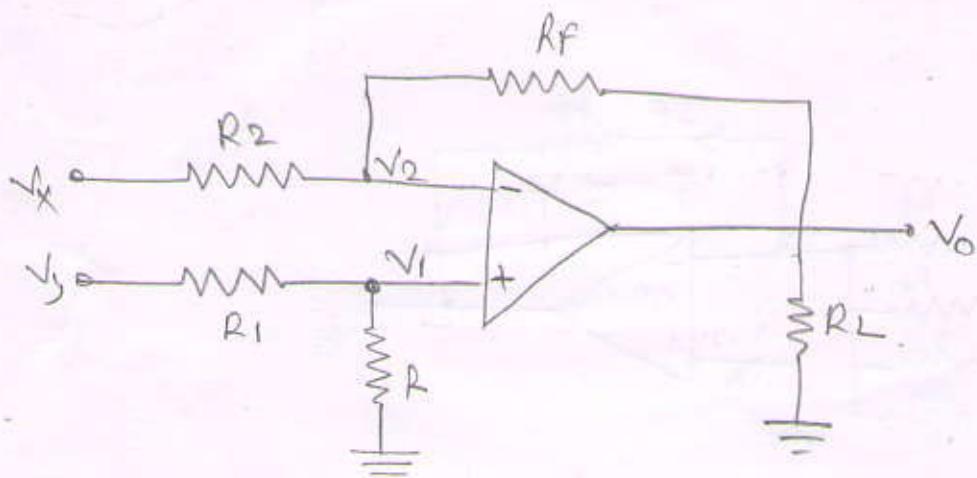

$$V_o = \frac{R_f}{R_1} [-V_y - V_x]$$

$V_x$  = Voltage at inverting terminal

$V_y$  = Voltage at non-inverting terminal

→ यह op-amp के gain की unity के लिए जापा दि

$$R_1 = R_f = R$$

$$V_o = V_y - V_x$$



Hence o/p Volt. is equal to the difference  
of I/p Voltages  $V_{dy}$  &  $V_{dx}$ .

Hence It is called Subtractor.  
Similarly we can increase the No. of Inputs.

$$(V_{dy} + V_{dx}) - V_{dx} = V_{dy}$$

Q3) Explain RC- phase shift oscillator using op-amp 741 IC.

Ans →

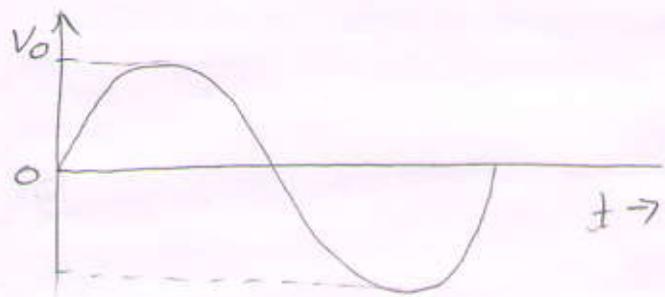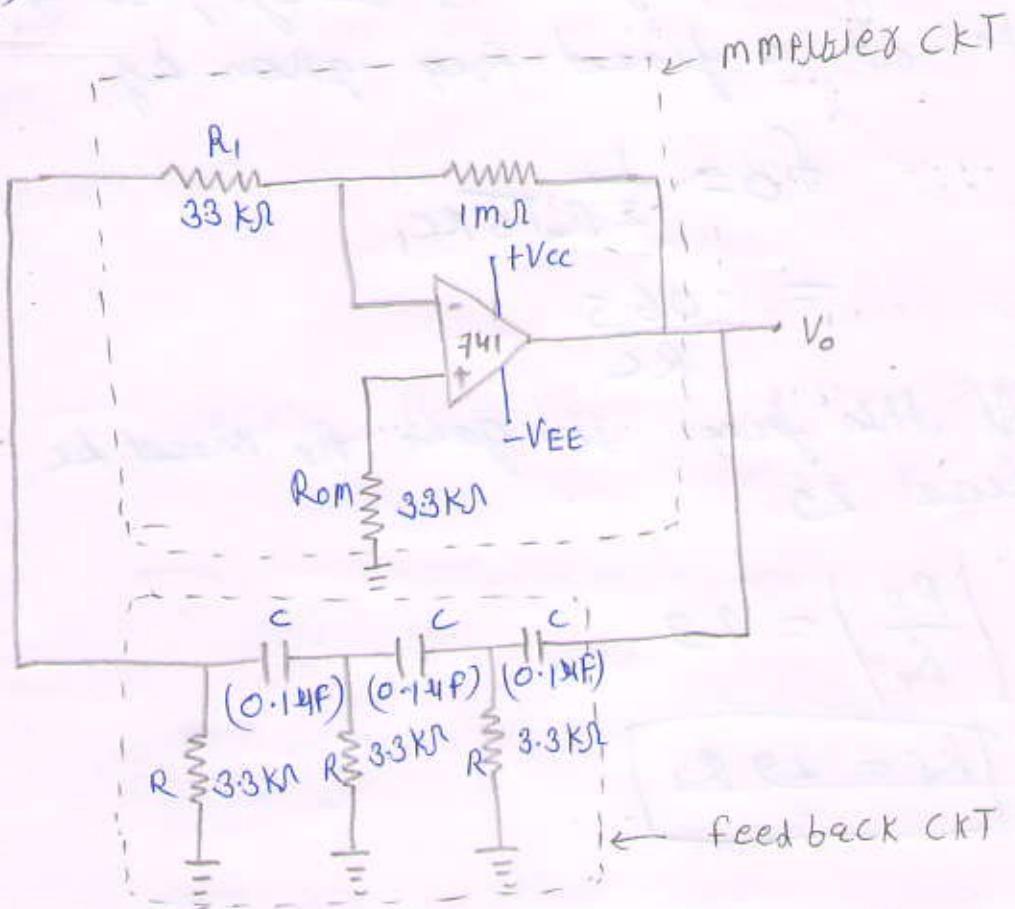

R-C Phase Shift oscillator में एक OP-AMP से तीन R-C cascade Network होते हैं। तीनों Cascade N/w feedback loop में होते हैं।

The f/b ckt is used to provides the f/b volt. from O/p Back to I/p of the Amplifier.

The O/p is used in the Inverting Mode, therefore any signal that appears at the Inverting terminal is shifted by  $180^\circ$  at the O/p. An additional  $180^\circ$  phase shift is required for oscillation.

It is provided by 3 R-C N/w

$\therefore$  1 R-C N/w gives  $60^\circ$  phase-shift. Hence  
3 R-C N/w gives  $180^\circ$  " "

$\therefore$  Gain of Amplifier is large, so ckt will oscillate at a fixed freq. given by

$$f_0 = \frac{1}{2\pi\sqrt{6RC}}$$

$$= \frac{0.65}{RC}$$

At this freq. The gain  $A_0$  must be at least 29.

$$\left| \frac{R_f}{R_i} \right| = 29$$

$$\boxed{R_f = 29 R_i}$$