

राजकीय पोलिटेक्निक महाविद्यालय कर्नाली  
विद्युत विभाग

II - Mid term test


Subject - Electrical Circuit theory

Code - EE 205


Max Marks - 15 Date - 18/01/2018

Attempt any three question.

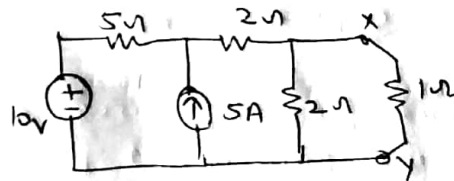Q.1) In fig, find the power loss in  $1\Omega$  resistor using Norton's theorem. (05) Marks



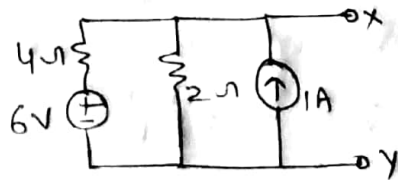Q.2) Find Millman's equivalent for the left of the terminals x-y as shown in fig. (05) Marks




Q.3) In the ckt of fig, find the current through the  $5\Omega$  resistor using the principle of superposition. (05) Marks



Q.4) State the theorem's theorem and explain it. (05) Marks

Q.1)

Ans.1)

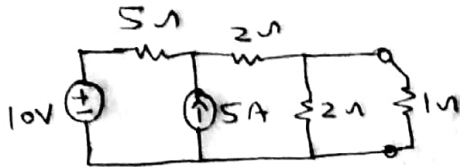

Remove the 1Ω resistor and short x-y



At node 1

$$\frac{V-10}{5} + I_{sc} = 5 \quad \text{--- ①}$$

$$I_{sc} = \frac{V}{2} \quad \text{--- ②}$$

From eq. ①

$$\frac{V-10}{5} + \frac{V}{2} = 5$$

$$0.7V = 7$$


$$V = 10V$$

put the value of V in eq. ②


$$I_{sc} = \frac{10}{2} = 5A$$

Q.2)

Ans.2)

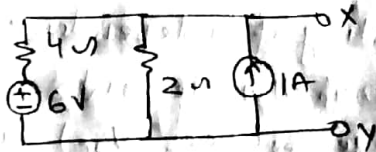

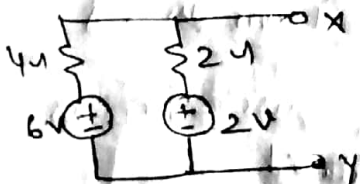First convert the current source of 1A to voltage source




Nillman's equivalent voltage

$$V = \frac{V_1 R_1 + V_2 R_2}{R_1 + R_2} = \frac{6 \times \frac{1}{4} + 2 \times \frac{1}{2}}{\frac{1}{4} + \frac{1}{2}}$$

$$= \frac{5}{2} \times \frac{4}{3} = \frac{10}{3} V$$
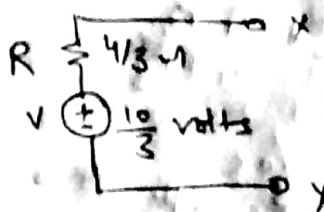
$$R = \frac{1}{\frac{1}{4} + \frac{1}{2}} = \frac{4}{3} \Omega$$




Q.3)

Ans.3)




Using superposition

replace voltage source by short circuit

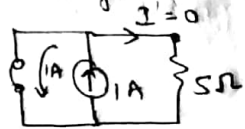

$I' = 0$  A (current through  $5\Omega$  resistor)

replacing current source by open ckt

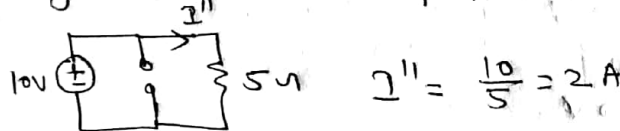

Using superposition


current through  $5\Omega$  resistor  $I_S = I' + I'' = 0 + 2 = \underline{2 \text{ Amp}}$

Q.4)


Ans.4)

Statement - Any linear active N/w consisting of independent or dependent voltage and current source and linear bilateral N/w elements can be replaced by an equivalent circuit consisting of voltage source ( $V_{oc}$ ) and a series resistance ( $R_{th}$ ).

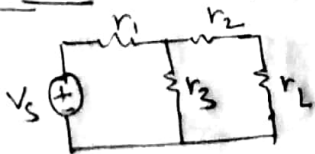
for Exam, - find the thevenin's eq. ckt. as shown in fig.



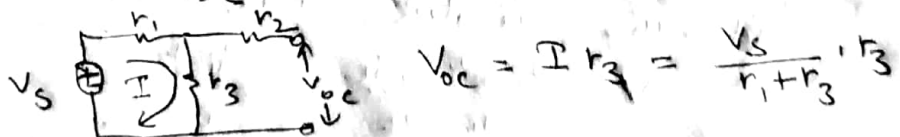find eq. voltage source,  $r_L$  is removed and  $V_{oc}$  is calculated



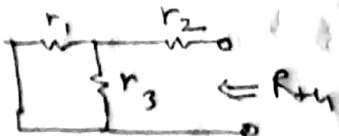
Next to find internal resistance (thevenin's resistance), the voltage source is removed



$$R_{th} = r_2 + (r_1 || r_3)$$

$$= r_2 + \frac{r_1 r_3}{r_1 + r_3}$$

thevenin's equivalent network

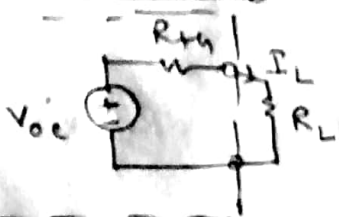

$$I_L = \frac{V_{oc}}{R_{th} + R_L} \text{ Amp}$$