

MODEL TEST PAPER
SUB CODE EE301 / EL 305
EE - III Year

- Q:1 : SCR & TRIAC are respectively
- Both are unidirectional
 - Both are bidirectional
 - SCR is unidirectional & TRIAC are bidirectional
 - SCR is bidirectional & TRIAC is unidirectional



[C]

Q:2 : what is holding current & Latching current?

→ Holding current :- minimum value of current that must be there to provide a path between anode & cathode to flow anode current to maintain SCR in on state. Below holding current SCR will be off.

Latching current :- min Anode current required to maintain a thyristor in on state immediately after SCR is triggered on. Its value is greater than holding current.

Q:3 what is the difference between SCR & TRIAC?

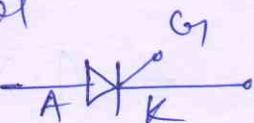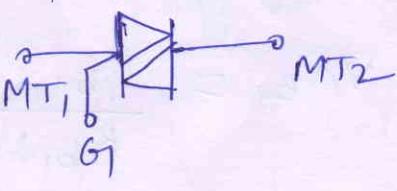
SCR	TRIAC
① symbol	symbol
	

- Available in Large ratings
- Available in Smaller ratings

- 3) SCR can be triggered by positive gate volt only.
- 4) It control DC power
- Triac can be triggered either by positive or negative gate voltage
- Control DC as well as AC power.

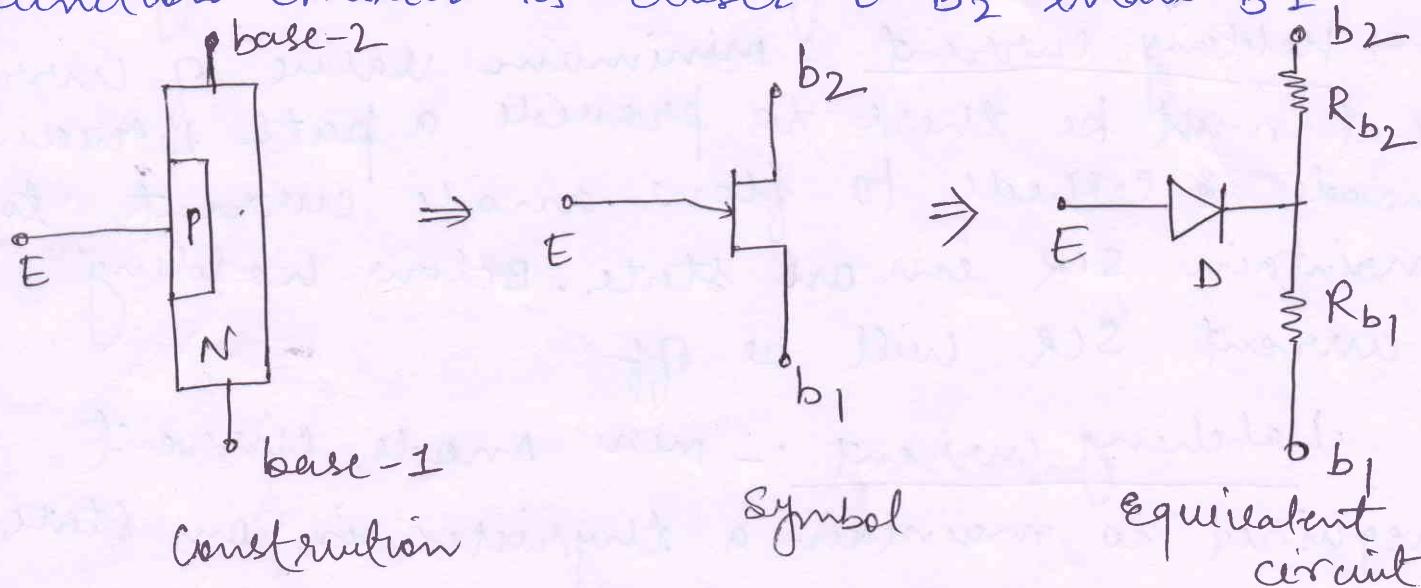Q. 3: Explain UJT construction, operation & application?

Ans:- UJT refers to unijunction transistor. It has 3 terminals Emitter & two bases i.e. B_1, B_2 . The base is formed by a lightly doped n-type bar of silicon. Emitter is of p-type heavily doped junction. Emitter is closer to B_2 than B_1 .




It is called unijunction transistor because there is single junction formed by embedding in of n-type Si base & p-type emitter.

When a volt V_{BB} is applied across the two base terminals B_1 & B_2 ; potential of point A w.r.t B_1 is given by

$$V_{AB_1} = \frac{R_{b_1} \cdot V_{BB}}{R_{b_1} + R_{b_2}} = \eta \cdot V_{BB}$$

$$\eta = \frac{R_{b_1}}{R_{b_1} + R_{b_2}} \rightarrow \text{Intrinsic stand off ratio} \rightarrow 0.5 - 0.8$$

UJT operation :-

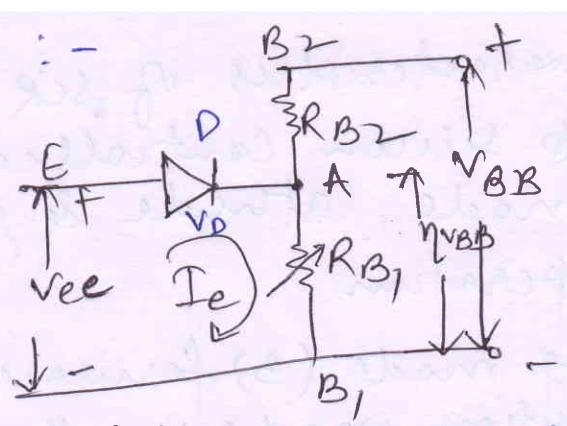

When volt V_{BB} is applied between base b_1 & b_2 than volt $V_A = nV_{BB}$ & this volt acts as R_B on diode D. if $V_{EE} < V_A$ there is no current flow in emitter due to Reverse biasing of diode. if $V_{EE} > nV_{BB} + V_D$ than current flow through diode D.


There are 3 regions in UJT

1. Cutoff region - No current flow in emitter circuit. and UJT is off in this state.
2. Negative resistance region - emitter volt is decreased to Valley point volt and emitter current is increased. Due to flow of current in b_1 , no of e^- is increased so resistance R_{B_1} is decreased. Since $R_B \propto e^{\frac{V}{n}}$ with volt \uparrow hence it is called negative resistance region. Flow of current into UJT emitter causes resistive value of R_{B_1} to \downarrow , allowing more current flow.
3. Saturation region

(3) Saturation Region:- Increasing V_{EE} keeps emitter voltage constant but emitter current increases

Application :-

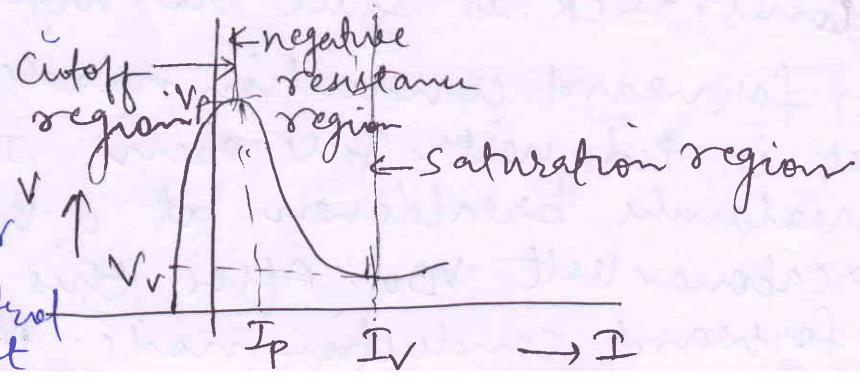- (1) used as a relaxation oscillator
- (2) used in phase control circuit



Q4 Explain V-I characteristics of SCR with graph?

Ans:- SCR refers to Silicon Controlled Rectifier. It has 3 terminals Anode, Cathode & gate. It has 3 basic modes of operation

- (A) Reverse Blocking mode (B) forward blocking mode
(C) forward conduction mode.

(A) Reverse blocking mode:- When cathode is made \uparrow wrt Anode & gate open the SCR is reverse biased


and small current of few mA will flow. This is R.B mode

Q.P. if reverse volt is tied to breakdown level V_{BR} , an avalanche breakdown occurs at J_1 & J_3 . J_2 is forward biased.

In this mode device offers high impedance state.

(B) forward Blocking mode \rightarrow when Anode is positive wrt cathode, & gate open. SCR is forward biased. J_1 , J_3 is forward biased and J_2 is R.B in this mode small forward leakage current flows. SCR is still in high impedance state.

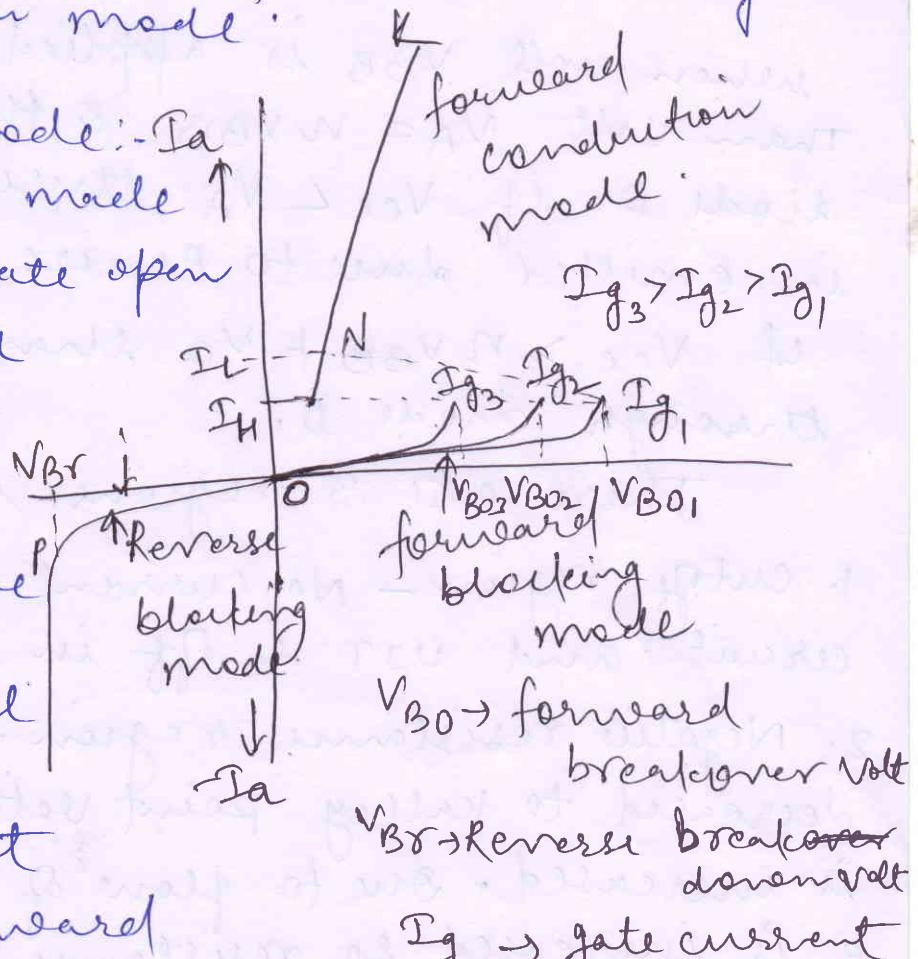(C) forward conduction mode:- when A-K forward volt is tied with gate open, J_2 will have an avalanche breakdown at a volt called forward breakdown volt V_{BO} . After this SCR entered into forward conduction mode. NK.



$V_{BO} \rightarrow$ forward breakdown volt
 $V_{BR} \rightarrow$ reverse breakdown volt
 $I_g \rightarrow$ gate current