

GOVERNMENT POLYTECHNIC COLLEGE BHILWARA

II MID TERM: 14<sup>th</sup> February 2018


II- Year Electronics

Maximum Marks: 15


EL- 202 Circuit Theory

All Questions are compulsory/. सभी प्रश्न अनिवार्य हैं

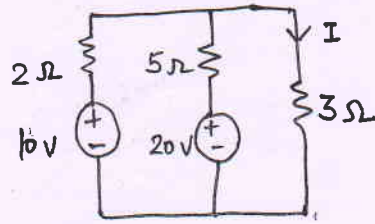
1. Define Tellegen's Theorem with an example/Tellegen के प्रमेय को उदाहरण के साथ स्पष्ट कीजिये [3 marks]
2. Calculate the current  $I$  in the circuit using Millman Theorem/ निम्नलिखित परिपथ में Millman प्रमेय की मदद से धारा  $I$  को ज्ञात कीजिये [3 marks]



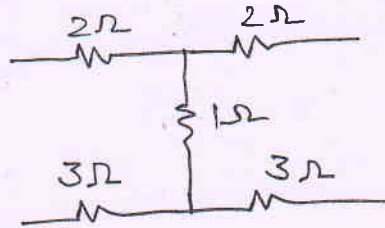3. Calculate all the Z parameters for the given circuit/ दिए गए परिपथ में सभी Z प्राचल ज्ञात कीजिये [3 marks]



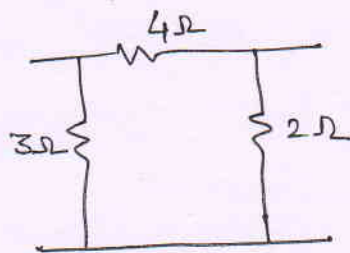4. Calculate all the Y parameter for the given circuit / दिए गए परिपथ में सभी Y प्राचल ज्ञात कीजिये [3 marks]



5. Calculate the value of  $h_{11}$  and  $h_{21}$  in terms of Z parameters / प्रचाल  $h_{11}$  एवं  $h_{21}$  को Z प्रचाल के रूप में ज्ञात कीजिये [3 marks]


## II- Mid Term (Electronics)

### EL-202 (Circuit Theory)
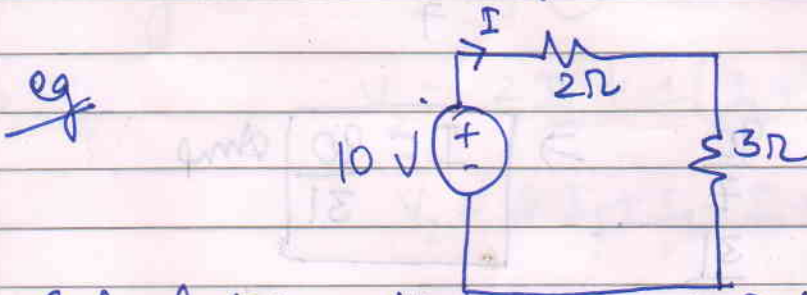
#### ① Tellegen's Theorem

According to this theorem the sum of the powers developed (delivered + absorbed) is zero at all instants of time.

This theorem is applicable irrespective of the fact whether the circuit is linear or non-linear, time variant or time invariant, causal or non causal.




Calculating the current  $I$  in the circuit  $I = \frac{10}{5} = 2 \text{ Amp}$

$$\text{Power delivered } P_D = -(10V \times 2 \text{ Amp}) = -20 \text{ Watts}$$

$$\text{Power absorbed } P_A = (2\Omega)^2 \times 2 \text{ Amp} + (2\Omega)^2 (3) = +20 \text{ Watts}$$

$$\text{Total power } P = P_D + P_A = +20 - 20 = \boxed{0 \text{ Watts}}$$

#### ② Given circuit

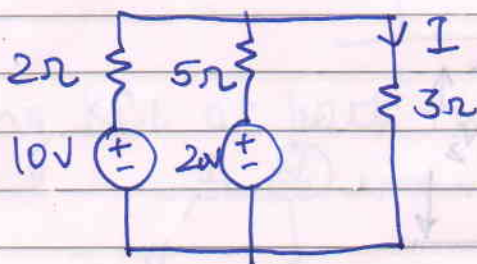

$$G_1 = 0.5 \text{ S}$$

$$G_2 = 0.2 \text{ S}$$

$$V_1 = 10 \text{ V}$$

$$V_2 = 20 \text{ V}$$


$$V_\eta = \frac{V_1 G_1 + V_2 G_2}{G_1 + G_2} = \frac{(10)(0.5) + (20)(0.2)}{0.7}$$



$$V_{\eta} = \frac{5+4}{0.7} = \boxed{\frac{90 \text{ volts}}{7}}$$

$$R_{\eta} = \frac{1}{G_1 + G_2} = \boxed{\frac{10 \Omega}{7}}$$


Millman's equivalent circuit

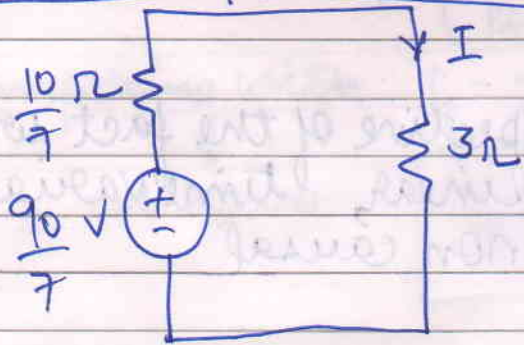


$$I = \frac{\frac{90}{7}}{\frac{10}{7} + 3}$$

$$I = \frac{\frac{90}{7}}{\frac{31}{7}} \Rightarrow \boxed{I = \frac{90}{31} \text{ amp}}$$

③ Given circuit

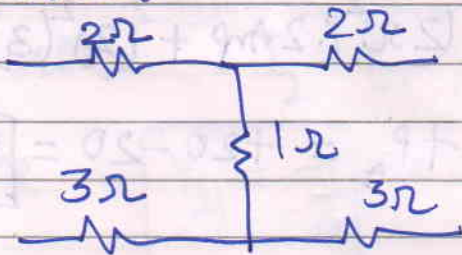

using KVL in both loops

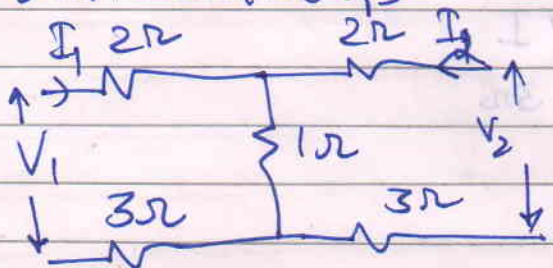

$$\frac{(3.0)(0) + (2.0)(0)}{7.0} = \frac{20V + 0V}{7.0} = \frac{20}{7}$$

$$V_1 = 2I_1 + 1(I_1 + I_2) + 3I_1$$

$$V_1 = 2I_1 + I_1 + I_2 + 3I_1$$

$$\text{or } V_1 = 6I_1 + I_2$$

comparing with  $V_1 = Z_{11}I_1 + Z_{12}I_2$

we have

$$Z_{11} = 6\Omega$$

$$Z_{12} = 1\Omega$$

using KVL in loop (2)

$$V_2 = 2I_2 + 1(I_1 + I_2) + 3I_2$$

$$V_2 = 2I_2 + I_1 + I_2 + 3I_2$$

$$V_2 = I_1 + 6I_2$$


comparing with  $V_2 = Z_{21}I_1 + Z_{22}I_2$

we have


$$Z_{21} = 1\Omega$$

$$Z_{22} = 6\Omega$$

(4) Given circuit

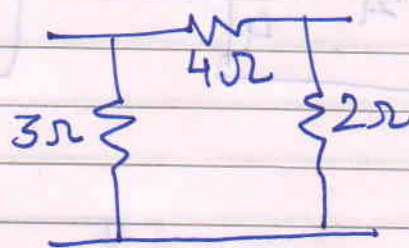

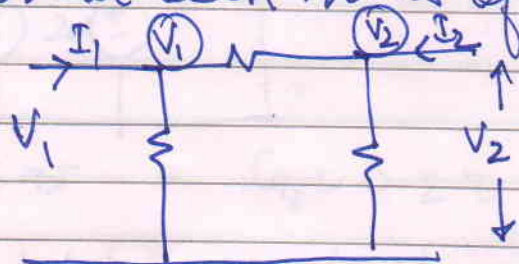applying KCL at both nodes of the circuit





For node 1:

$$I_1 = \frac{V_1}{3} + \frac{V_1 - V_2}{4} + IS = 0$$

$$\text{or } I_1 = V_1 \left( \frac{1}{3} + \frac{1}{4} \right) - \frac{V_2}{4} + IS = 0$$

$$\Rightarrow I_1 = \left( \frac{7}{12} \right) V_1 + \left( -\frac{1}{4} \right) V_2$$

Comparing with  $I_1 = Y_{11} V_1 + Y_{12} V_2$

we have

$$Y_{11} = \frac{7}{12} \text{ } \Omega$$

$$Y_{12} = -\frac{1}{4} \text{ } \Omega$$

For node 2:

$$I_2 = \frac{V_2}{2} + \frac{V_2 - V_1}{4}$$

$$I_2 = -\frac{V_1}{4} + V_2 \left( \frac{1}{2} + \frac{1}{4} \right)$$

$$I_2 = \left( -\frac{1}{4} \right) V_1 + \left( \frac{3}{4} \right) V_2$$

Comparing with

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

we have

$$Y_{21} = -\frac{1}{4} \text{ } \Omega$$

$$Y_{22} = \frac{3}{4} \text{ } \Omega$$

⑤ h-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

Z parameters

$$V_1 = z_{11} I_1 + z_{12} I_2 \quad \text{--- (3)}$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \quad \text{--- (4)}$$

using eq<sup>n</sup> (3) to calculate  $I_2$

$$I_2 = \frac{V_1 - z_{11} I_1}{z_{12}}$$

using in eq<sup>n</sup> (4)

$$V_2 = z_{21} I_1 + z_{22} \left( \frac{V_1 - z_{11} I_1}{z_{12}} \right)$$

$$z_{12} V_2 = z_{12} z_{21} I_1 + z_{22} V_1 - z_{11} z_{22} I_1$$

$$\text{or } z_{22} V_1 = (z_{11} z_{22} - z_{12} z_{21}) I_1 - z_{12} V_2$$

$$\text{or } V_1 = \left( \frac{\Delta z}{z_{22}} \right) I_1 + \left( \frac{-z_{12}}{z_{22}} \right) V_2$$

Comparing with eq<sup>n</sup> (1)

$$\boxed{h_{11} = \frac{\Delta z}{z_{22}}}$$

Q.A

(P. D. Upadhyay)  
Electronics