

EL-205 (Digital Electronics)

Question-Paper

Q-1 Q) State any two advantages of digital electronics

(डिजिटल इलेक्ट्रॉनिक्स के दो लाभ बताओ)

b) Convert into standard SOP expression

मानक SOP में परिवर्तित कीजिए

$$AB + BC + CA$$

(5)

Q-2 (a) Simplify using K-map

$$f = \sum m(0, 1, 3, 4, 5, 6, 13) + d(11, 12, 14, 15)$$

(b) Prove using Boolean Algebra

$$A + A\bar{B} + A\bar{B}C = A$$

(5)

Q-3

a) write truth table of 2-input EX-NOR gate
(2-input EX-NOR गेट की सत्य तालिका बनाओ)

b) Describe DeMorgan's theorem

(दमोर्गन त्रिमयी का वर्णन कीजिए)

(5)

Q-4

a) Write symbol of each gate (minimum = 7 gate)

b) Draw EX-NOR gate by using NAND gate. (5)

Attempt Any three →

Lecture - PKT

ANSWER-SHEET

Q-1 - a) State any two advantages of digital electronics

- Ans - i) An advantage of digital circuit is that signals represented digitally can be transmitted without degradation due to noise
ii) Each digit in digital circuit is handled by the same kind of hardware resulting in an easily scalable

b) $SOP = AB + BC + CA$

↓ Convert into ~~pos form~~ standard SOP

$$= ABC(C+\bar{C}) + BC(A+A\bar{A}) + CA(B+B\bar{B})$$

$$= ABC + A\bar{B}C + BCA + BC\bar{A} + CAB + CA\bar{B}$$

$$= 1 \cdot 1 \cdot 1 + 1 \cdot 1 \cdot 0 + 1 \cdot 1 \cdot 1 + 0 \cdot 1 \cdot 1 + 1 \cdot 1 \cdot 1 + 1 \cdot 0 \cdot 1$$

$$= m \sum (3, 5, 6, 7) \quad (\text{minterm})$$

Simplify using k-map

$$F = \sum m_i (0, 1, 3, 4, 5, 6, 13) + d(11, 12, 14, 15)$$

Ans - this is four variable (ABCD) k-map then $2^4 = 16$

Box in k-map,

Putting digit '1' in box giving in minterm

Putting 'X' in box giving Don't care term (11, 12, 14, 15)

(P.T.O.)

K-map

		$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
		00	01	11	10
		$\bar{A}\bar{B}$	00	01	11
$\bar{A}\bar{B}$	00	1	1	1	0
$\bar{A}B$	01	1	1	0	1
$A\bar{B}$	11	X	1	-X	-X
AB	10	0	0	X	0


2

There are two total Four group of one digit - 1
 (3 group of 4-box) + 1 group of 2-box

$$Y = \bar{A}\bar{C} + AB + BD + \bar{A}\bar{B}D$$

K-map is used for minimized of number of logic gates (minimization technique)

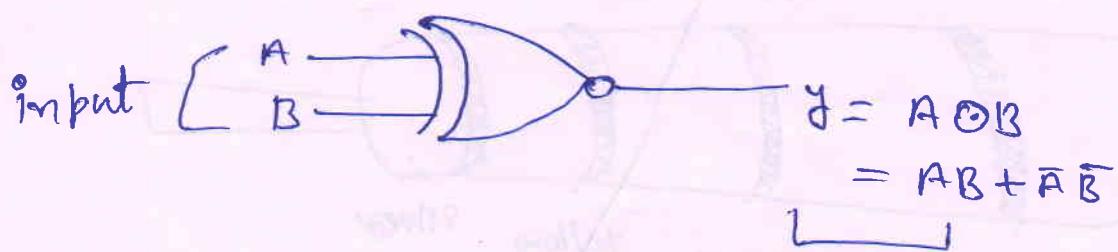Q-3] q) Write truth table of 2-input EX-NOR gate
 Sol] - symbol of EX-NOR gate



Truth table (सत्यसिद्धान्त)

Input		OUTPUT
A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

(P.T.O)

(3)

b) Describe De Morgan's theorem

Sol] The complement of the sum of two or more variables is equal to product of the complements of the variables

as

$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

The complement of the product of two or more variables is equal to sum of the complements of the variables

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

Q-4)

a) write symbol of each gate

Sol]

Name of gate

Symbol

AND

=



$$Y = A \cdot B$$

OR

=



$$Y = A + B$$

NAND


=



$$Y = \overline{A \cdot B}$$

NOR

=

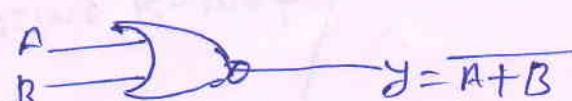

$$Y = \overline{A + B}$$

EX-OR


=



$$Y = A \oplus B = A\bar{B} + \bar{A}B$$

EX-NOR

=

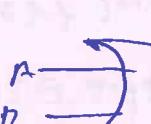

$$Y = A \odot B = AB + \bar{A}\bar{B}$$

NOT




$$\bar{A}$$

(P.T.O)

b) Draw EX-OR Gate by using NAND gate (4)

Sol]

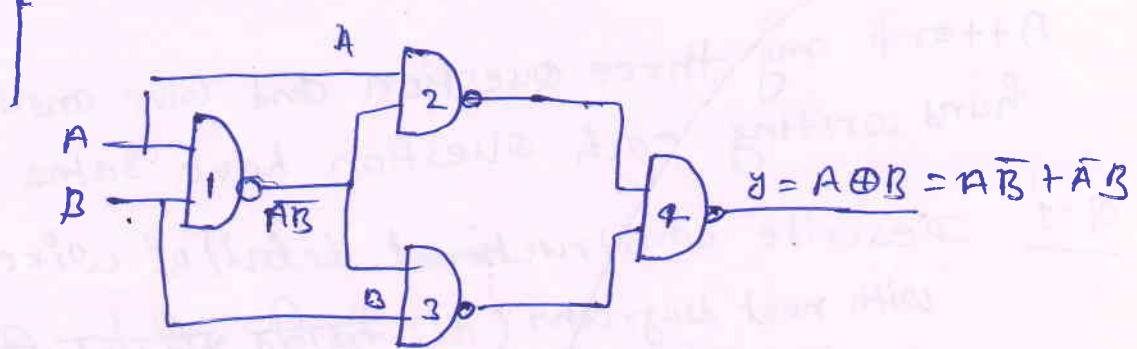

Total Four NAND Gate S equiv to make (design)
the EX-OR gate

Ans

Y = $\bar{A}B + A\bar{B}$

(Satisfactory)