

GOVERNMENT POLYTECHNIC COLLEGE BHILWARA

I MID TERM: 27TH November 2017

III- Year Electronics

Maximum Marks: 15


Attempt all questions/ सभी प्रश्नों का उत्तर देना अनिवार्य है

1. What is an oscillator? What are different types of oscillators? [2 marks]
2. Explain any 1 biasing method of FET Amplifier [3 marks]
3. Describe the circuit diagram and working of any 1 LC Oscillator [3 marks]
4. Calculate the **Voltage gain** and **Current Gain** of a Common Source Amplifier. [3 marks]
5. How does the **Voltage Gain** of amplifier changes at low and high frequency? Write the formulae. [4 marks]

SOLUTIONS

1st Mid-Term (EL-301) (27/11/2017)

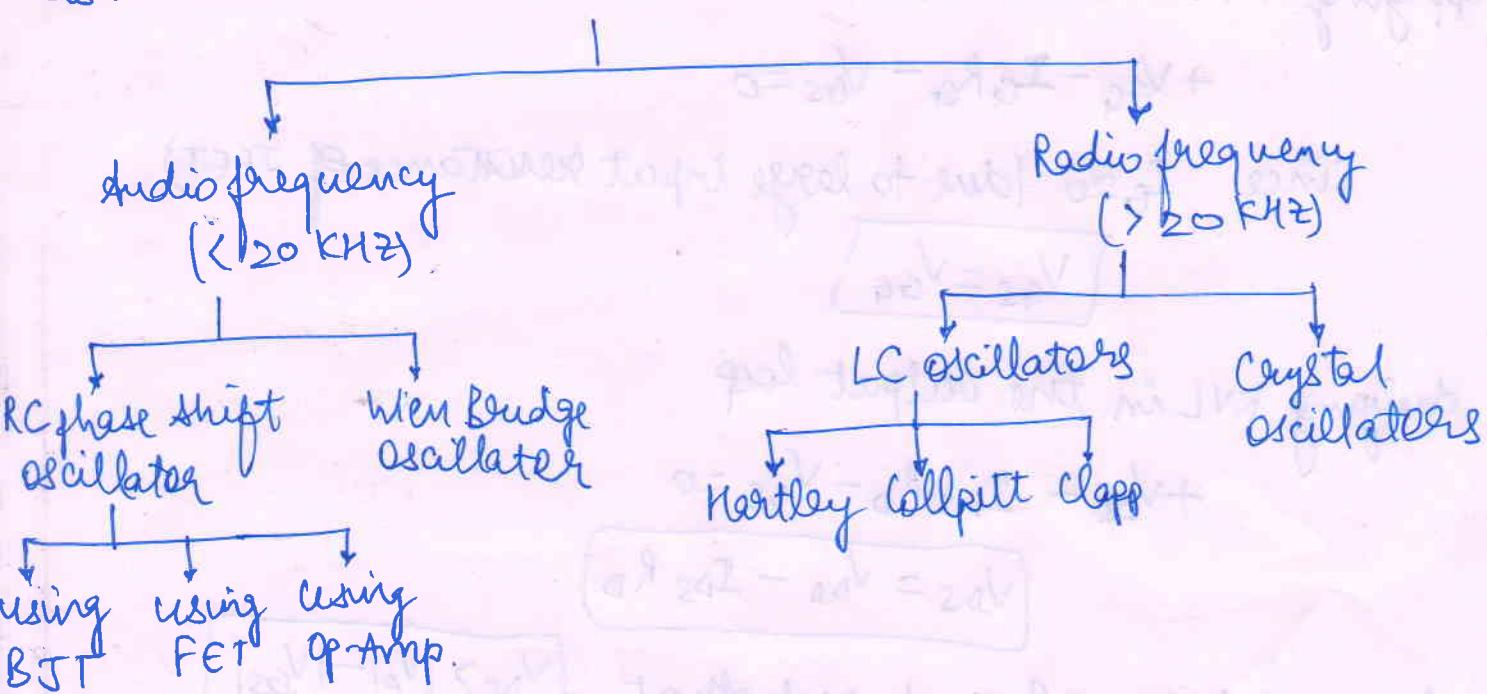
- ① An oscillator is a circuit which generates an AC waveform without using an AC input.
- Oscillators always produce sinusoidal waveforms.
- The circuits which generate non-sinusoidal waveforms such as square wave, triangular wave, etc. are called waveform generators.
- On the basis of frequency of operation, oscillators are classified as:



2) Biasing Method of FET Amplifier

Gate Bias

The circuit used for such biasing is:

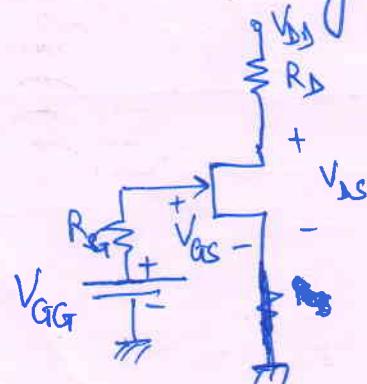

V_{DD} : Drain Supply

It is used to provide the drain current (I_{DS})

→ V_{DD} should be (+ve) for n-channel JFET

V_{DD} should be (-ve) for p-channel JFET

→ V_{GG} : Gate Supply

It maintains the gate channel junction in reverse bias and thus I_{DS} is controlled.

V_{GG} should be (+ve) for p-channel JFET

(-ve) for n-channel JFET

Applying KVL in the input loop

$$+V_{GG} - I_G R_G - V_{GS} = 0$$

Since $I_G \approx 0$ (due to large input resistance of JFET)

$$V_{GS} = V_{GG}$$

Applying KVL in the output loop

$$+V_{DD} - I_{DS} R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_{DS} R_D$$

R_D should be selected such that

$$V_{DS} > |V_P| - |V_{GS}|$$

For the above condition JFET operates in saturation region.


Drawback

It requires two biasing supplies.

③ LC oscillator

HARTLEY OSCILLATOR

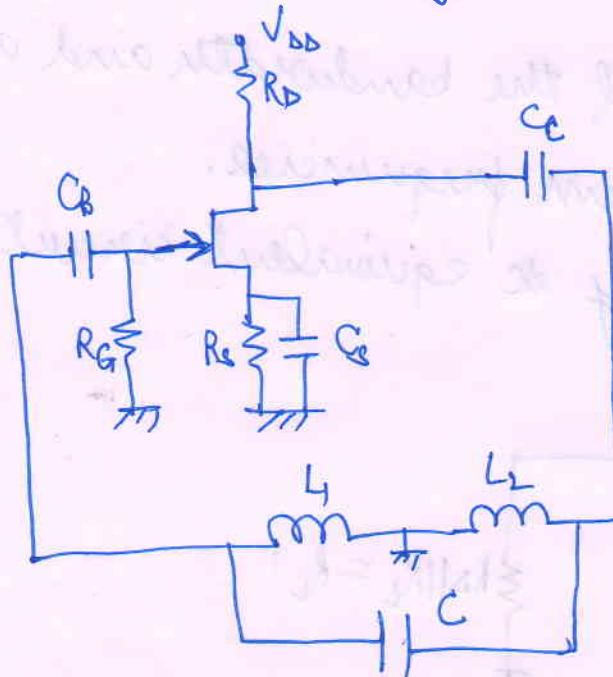- It consists of a Common source FET amplifier and an LC feedback network
- The CS amplifier provides a phase shift of 180° between the input and output voltage waveforms
- The LC feedback network provides an additional phase shift of 180° . therefore the total phase shift around the loop becomes 360° , thereby satisfying Barkhausen's criteria




C_B and C_F prevents the shorting and drain and gate with respect to ground.

- The frequency of oscillation is given as:


$$f_o = \frac{1}{2\pi\sqrt{(L_1+L_2)C}}$$

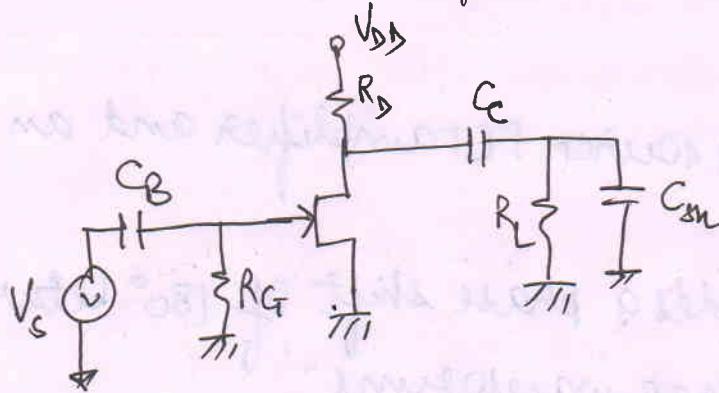④ A common source amplifier can be shown as:




For the above circuit the source self bias configuration maintains the JFET in saturation region.

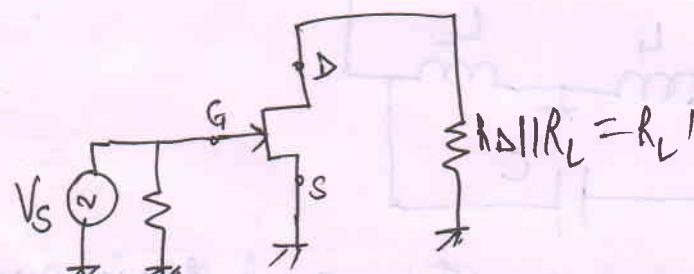- C_B and C_m can be considered as short circuit at medium frequencies
- C_m is used to control the bandwidth and acts as open circuit at medium frequencies.
- The medium frequency dc equivalent circuit can be shown as:



The small signal model can be shown as,

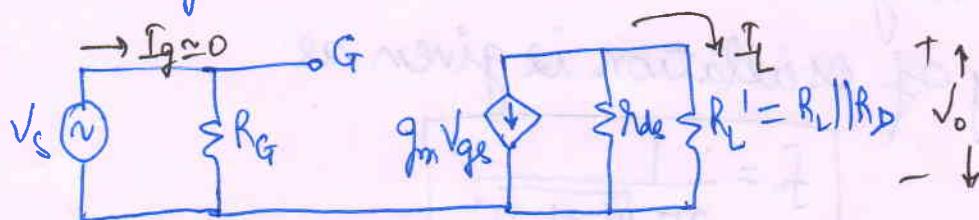

(i) Current Gain

$$A_I = \frac{I_L}{I_g}$$

Since $I_g \approx 0$, Hence $A_I \approx \infty$

(ii) Voltage Gain

$$\frac{V_o}{V_i} = A_{v0}$$

$$V_o = -g_m V_{gs} (\rho_{dss} || R_L')$$

$$V_i = V_{gs}$$

Hence $A_{v0} = -g_m (\rho_{dss} || R_L')$

5 For an FET amplifier the Gain at low frequency is given as:

$$A_{vL} = \frac{A_{vm}}{1 - j\left(\frac{f_L}{f}\right)}$$

or

$$|A_{vL}| = \frac{|A_{vm}|}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

$$\angle A_{vL} = 180^\circ + \tan^{-1} \left(\frac{f_L}{f} \right)$$

The gain of an amplifier decrease at low frequencies due to the effect of large capacitors such as C_B , C_C and C_S
→ Similarly the gain at high frequency is given as:

$$A_{vH} = \frac{A_{vm}}{1 + j\left(\frac{f}{f_H}\right)}$$

$$|A_{vH}| = \frac{|A_{vm}|}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$\angle A_{vH} = 180^\circ - \tan^{-1} \left(\frac{f}{f_H} \right)$$

(A)
 (P.D. Upadhyay)