


# MODEL TEST PAPER

SUB CODE : 307

Attempt any <sup>EL III year</sup> 5 questions

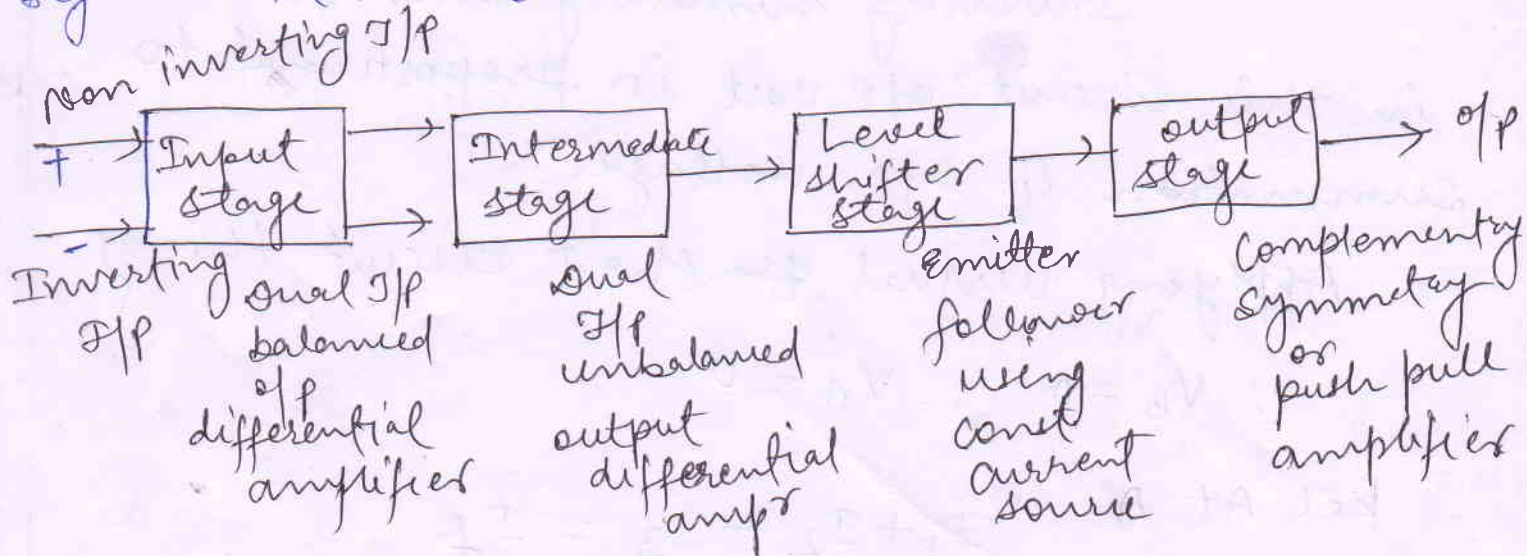Q:1 what is op-Amp. explain its block diagram? 174

it is high volt. gain direct coupled amplifier which can perform operation on analog signals. it is available as IC 741.




## op-Amp block diagram

I/P stage is dual i/p balanced o/p differential amp. It provides volt gain & I/P impedance.

Next stage is dual i/p unbalanced o/p differential amplifiers. Two diff<sup>r</sup> amplifier are used to achieve high volt gain. Its o/p has DC voltage. if this DC volt reaches at o/p than it creates distortion in final o/p. so a level shifter stage is used to eliminate DC present in o/p of intermediate stage. Level shifter stage has high i/p impedance which prevents loading effect on intermediate stage. o/p stage is complementary symmetry or push pull power amplifiers. so that op-Amp can provide large AC power to load & low o/p resistance.

Q:2 How op-Amp can be used as Adder? explain!

Ans: -

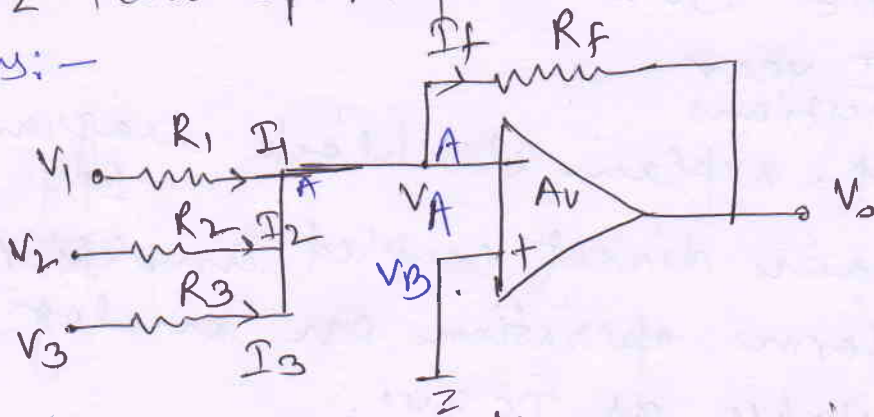

Inverting summing amplifier  
in this circuit op volt is proportional to  
summation of 2/p voltages

Applying virtual ~~to~~ short circuit theory

$$\therefore V_B = 0 \quad \therefore V_A = 0$$


KCL At A  $I_1 + I_2 + I_3 = I_f$

$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} + \frac{V_3 - 0}{R_3} = \frac{0 - V_0}{R_f}$$

$$V_0 = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

if  $R_1 = R_2 = R_3 = R$
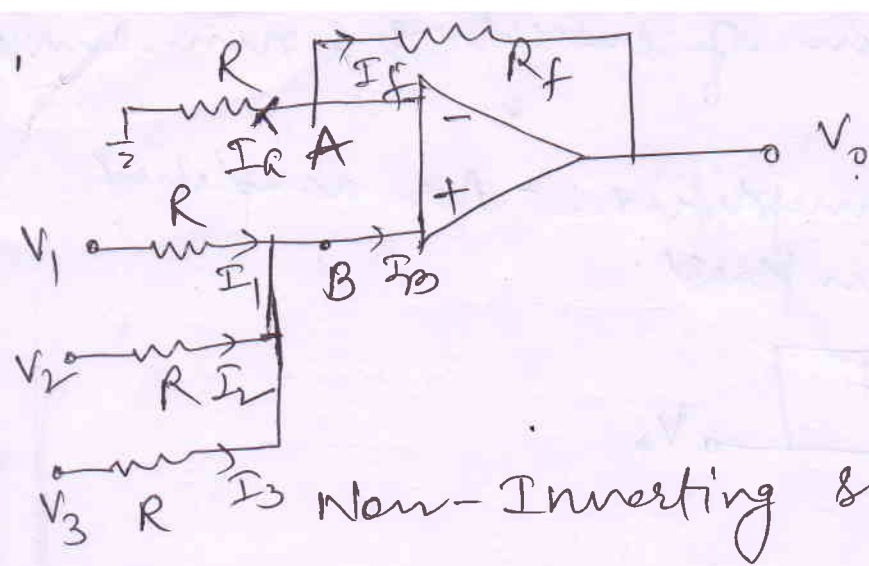
$$V_0 = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$



Non-Inverting summing amplifier.

Applying KCL At node B

$$\frac{V_1 - V_B}{R} + \frac{V_2 - V_B}{R} + \frac{V_3 - V_B}{R} = 0$$

( $\because$  IP impedance of op Amp is very high)

$$V_B = \frac{V_1 + V_2 + V_3}{3}$$

Now According to virtual ground theory

$$V_A = V_B$$

Apply KCL at node A  $\Rightarrow I_a + I_f = 0$


$$\frac{V_B - 0}{R} + \frac{V_B - V_0}{R_f} = 0 \Rightarrow V_B \left[ \frac{R_f + R}{R \cdot R_f} \right] = \frac{V_0}{R_f}$$

$$V_0 = \left( 1 + \frac{R_f}{R} \right) \left( \frac{V_1 + V_2 + V_3}{3} \right)$$

$$\text{Amplification factor} = \frac{1}{3} \left( 1 + \frac{R_f}{R} \right)$$

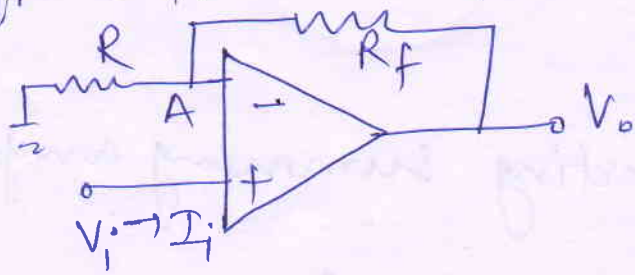2.3 Calculate the gain of inverting & non-inverting amplifier?

Non inverting amplifier :- An amplifier whose o/p & i/p are in phase.



R & Rf creates negative feedback.  
 Due to negative feedback  
 $V_d \approx 0$  Very small

$$V_d \approx 0$$


$$V_i - V_A = 0$$

$$V_A = \frac{V_o \times R}{R + R_f}$$

$$V_i = \frac{V_o \times R}{R + R_f}$$

$$V_o = \left(1 + \frac{R_f}{R}\right) \cdot V_i \Rightarrow \boxed{A_{CL} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R}}$$

$A_{CL} \rightarrow$  closed loop gain

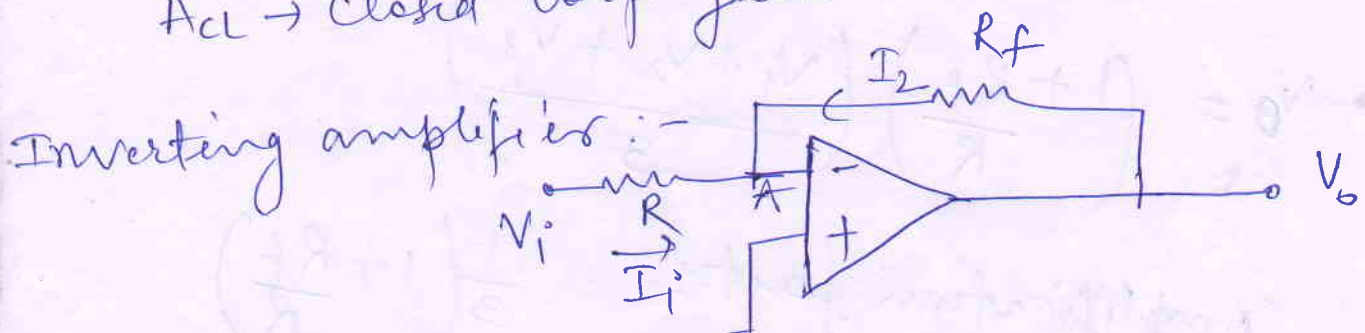

An amplifier whose i/p & o/p are out of phase by  $180^\circ$ .

$R$  &  $R_f$  creates -ve feedback.

Due to -ve feedback virtual short circuit will be present b/w two op nodes.

$$\therefore V_A = 0$$

$$\text{KCL at node A} \rightarrow I_1 + I_2 = 0$$


$$\frac{V_i - V_A}{R} + \frac{V_o - V_A}{R_f} = 0$$

$$V_o = -\frac{R_f}{R} \cdot V_i$$

close loop gain

$$A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R}$$

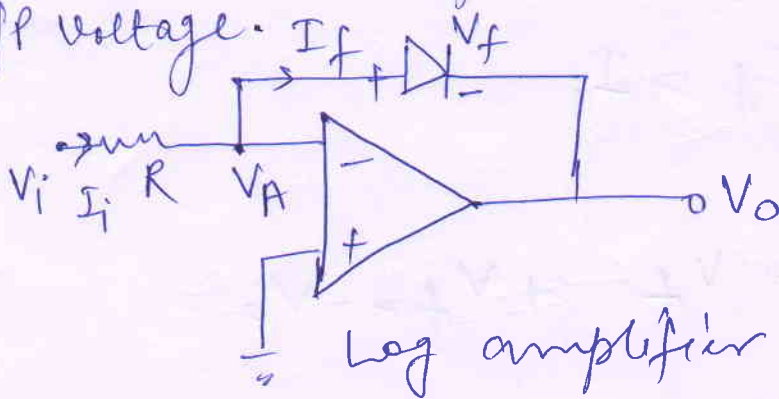Q:4 → Explain log amplifier? proportional to  
 In this amplifier op volt is logarithmic  
 of i/p voltage.



Log amplifier  
 Current for p-n Junction diode

$$I_f = I_0 (e^{V_f/nV_T} - 1)$$

$I_f$  = forward bias current

$V_f$  = forward volt drop

$$V_T = \frac{kT}{q} = \text{Boltzmann}$$

$I_0$  = saturation current

for  $\beta \gg 1 \Rightarrow \eta = 1$

for  $\beta \gg 1 \Rightarrow \eta = 2$

$$I_f = I_0 e^{V_f / \eta V_T}$$

$$\left( \because \frac{V_f}{\eta V_T} \gg 1 \right)$$

$$V_f = \eta V_T \log \left( \frac{I_f}{I_0} \right)$$

$$I_f = \frac{V_i - V_A}{R}$$

Apply virtual ground theory

$$V_A = 0$$

$$I_i = \frac{V_i}{R}$$

Apply KCL At A

$$I_f = I_i$$

$$0 - V_o = V_f \Rightarrow V_f = -V_o$$

$$V_o = -\eta V_T \log \left( \frac{V_i}{R \cdot I_0} \right)$$

$$\boxed{V_o \propto \log V_{in}}$$

श्रीमती

मीनाक्षी विमल