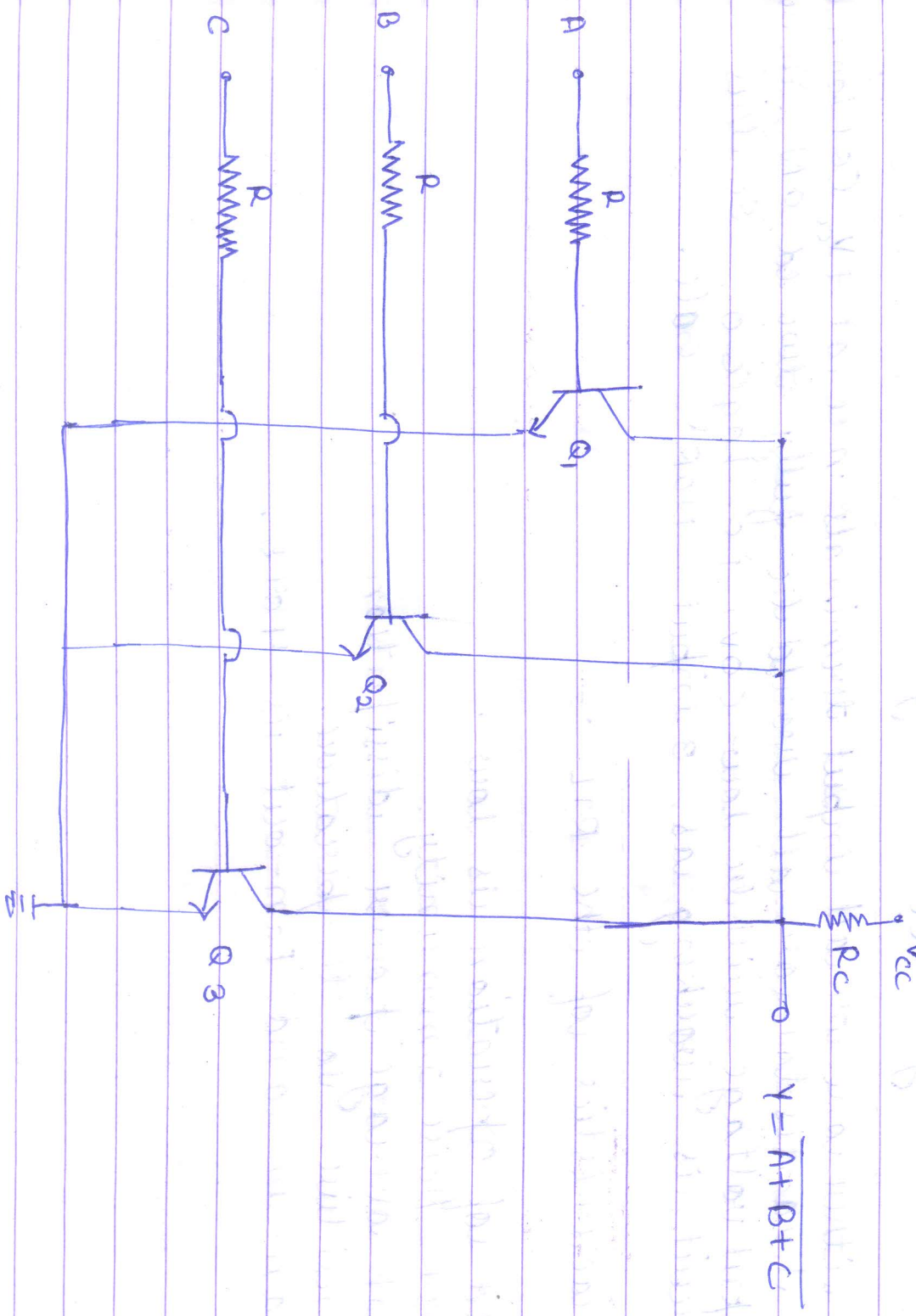


Ques. 1. Explain the working of a 3 input RTL NOR gate (Resistor Transistor logic) NOR gate also write its main characteristics? — (5)

Ans 1



Basic Diagram of RTL NOR gate

Working :- When the inputs A, B and C are at 0V (i.e. logic 0), the transistors are turned OFF. Hence the output goes to high (+V_c) i.e. logic 1.

→ If either one or all input terminals are at +V_c (i.e. logic 1), and transistor are all would be fully turned ON, therefore output voltage will be low (0V) i.e. logic 0. So this circuit is working as 3 input NOR gate.

Characteristics of the RTL :-

- 1) Speed of operation is low.
- 2) Poor Noise Immunity.
- 3) High average power dissipation.
- 4) Sensitive to temperature.
- 5) Fan-in and Fan-out is 4 or 5.



Ques 2. Design a NOT, AND, OR gates using universal gates. (6)


Ans 2. a) NOT gate :-

IP	OP
0	1
1	0




Symbol

Truth Table

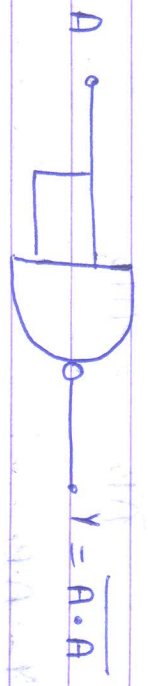

$Y = \bar{A}$

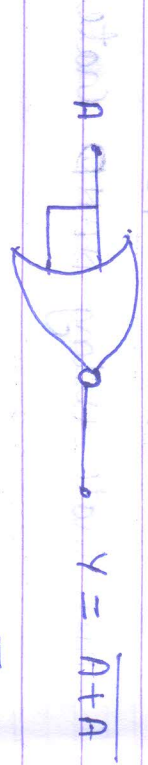

$Y = \bar{A}$



NOT gate using NAND gate

NOT gate using NOR gate

(Handwritten signature)

(b) AND gate :-

i/p		o/p
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

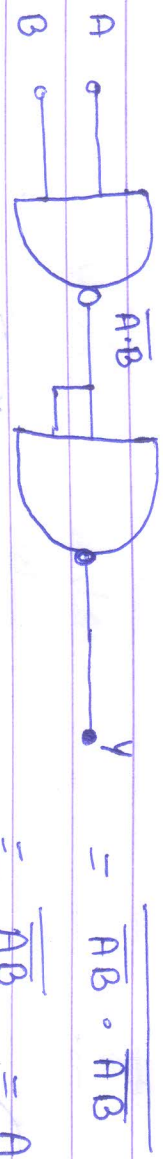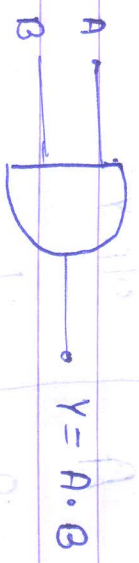


$$Y = \overline{\overline{A \cdot B} \cdot \overline{A}}$$

$$= \overline{\overline{A \cdot B} \cdot \overline{A}}$$

$$= A \cdot B$$

AND gate using NAND gate

$$Y = A \cdot B$$

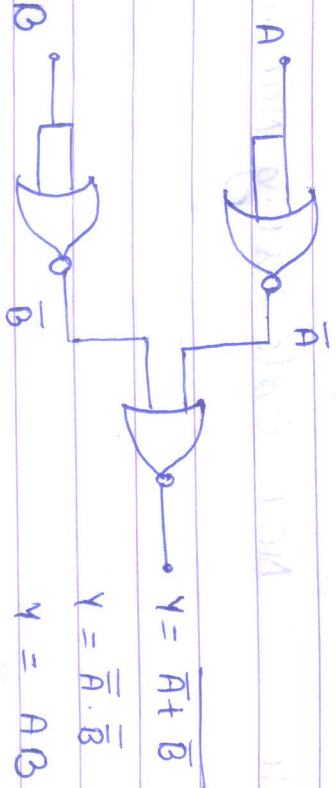

$$Y = \overline{\overline{A + B} \cdot \overline{A}}$$

$$= \overline{\overline{A + B} \cdot \overline{A}}$$

$$= A \cdot B$$



AND gate using NOR gate

sg

(c) OR Gate:-

i/p o/p

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

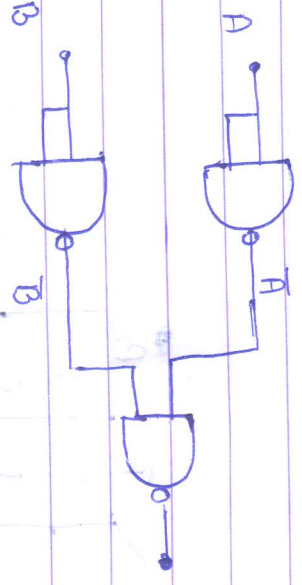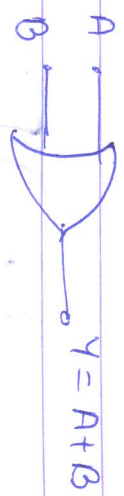


$$Y = \overline{H \cdot H}$$

$$Y = \overline{\overline{A + B}}$$

$$Y = A + B$$

OR gate using NAND gate

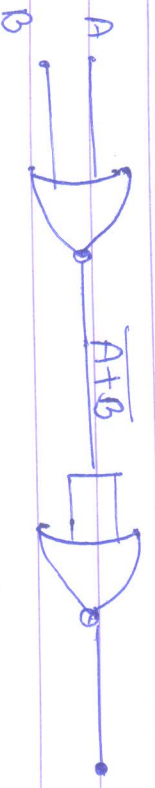

$$Y = \overline{\overline{A + B} + \overline{A + B}}$$

$$= (\overline{\overline{A + B}}) \cdot (\overline{\overline{A + B}})$$

$$= (A + B) \cdot (A + B)$$


OR gate using NOR gate

$$Y = (A + B)$$

Ques 3. Draw the Truth Table and logic Symbol of Ex-OR gate.
 Ex-NOR gate. Find the expression of Result using K-map.


(4)

Ans. Ex-OR :-

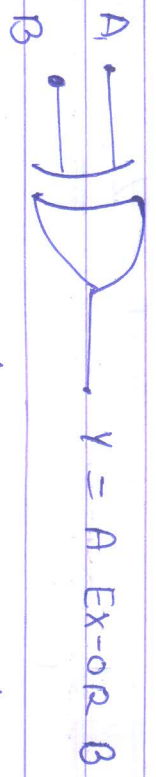

Symbol of Ex-OR gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

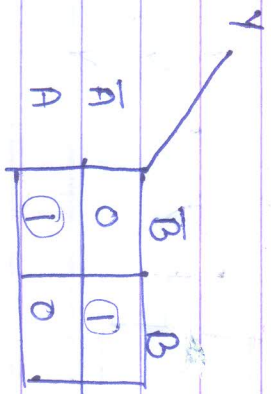


$$Y = \bar{A}B + A\bar{B}$$

$$Y = A \oplus B$$

Truth Table of Ex-OR gate


~~6~~

Ex-NOR :-

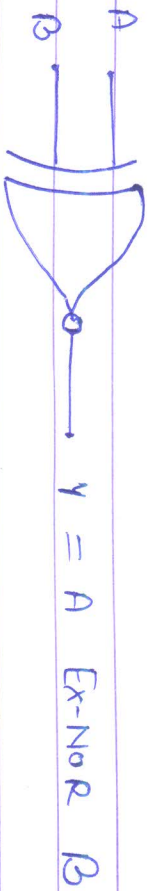

Symbol of Ex-NOR gate

i/p		o/p
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

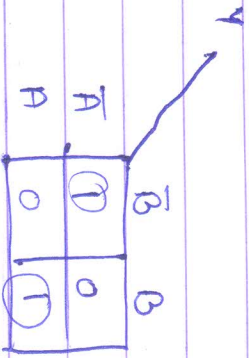

$$Y = AB + \bar{A}\bar{B}$$

$$Y = A \oplus B$$

Truth Table of Ex-NOR gate

~~Pravin~~

(PRIYANKA SAINI)

Lecturer Electronics

GWPC, Agner