

All Questions are compulsory/ सभी प्रश्न अनिवार्य हैं

**MULTIPLE CHOICE QUESTIONS**

- Which of the following quantity cannot be measured using Superposition Theorem: [1/2 marks]  
 [a] Current [b] Voltage [c] Power [d] None of these
- Kirchoff's Current Law can be applied on which parts of a circuit: [1/2 marks]  
 [a] Loop [b] Node [c] Branch [d] All of these
- The given figure represents which type of circuit element: [1 marks]  
 [a] Voltage Dependent Voltage Source  
 [b] Current Dependent Voltage Source  
 [c] Current Dependent Current Source  
 [d] Voltage dependent current source




**SHORT ANSWER QUESTIONS**

- Define Kirchoff's Voltage Law [1/2 marks]
- Define Tellegen's Theorem [1/2 marks]
- Draw diagrams of Independent and Dependent Sources [1 marks]
- How do you understand by Thevenin Voltage and Thevenin Resistance of a circuit [1 marks]

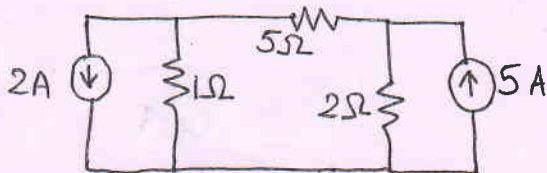
**LONG ANSWER QUESTIONS**

- Find the current in the 5 ohm resistor using KCL [3 marks]



- Convert the given circuit from one form to another [3 marks]


a. Star to Delta

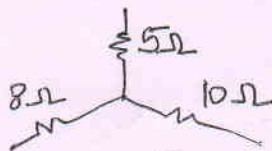

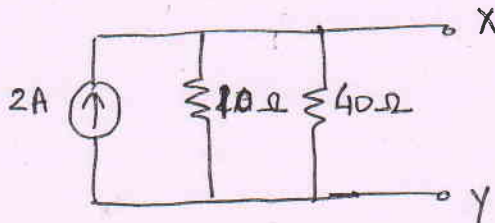b. Delta to Star



- Calculate the Thevenin's Equivalent circuit to the left of XY in the given circuit [4 marks]



1) (c) Power

Superposition Theorem is applicable for linear quantities. Since power is a non-linear function of  $V$  and  $I$ , hence it cannot be used for power calculation.

2) (b) Node





In a circuit currents (incoming and outgoing) can be added at a node only, hence KCL is applicable only at a node.

3) (b) Current dependent voltage source


Since the voltage is a linear function of current, hence the given source is a current dependent voltage source.

4) Kirchhoff's voltage law is based on the law of conservation of energy. This law states that the algebraic sum of voltages in a closed loop is zero.

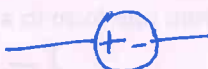5) Tellegen's Theorem states that the sum of the powers developed in a closed circuit is zero. This theorem is applicable for linear as well as non linear circuits, Time Variant as well as Time Invariant circuits.

6) Independent voltage source   $v = 10 \text{ volts}$   
 Independent current source   $i = 5 \text{ Amperes}$   
 Dependent voltage source   $v = Kv, \text{ or } v = Ki,$   
 Dependent current source   $i = Kv, \text{ or } i = Ki,$

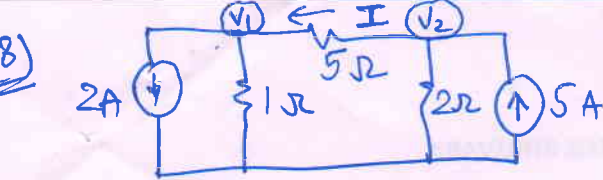7) Thevenin voltage is the open-circuit voltage across the terminals of a network (whose Thevenin equivalent is to be calculated).  
Thevenin Resistance is the resistance of a network when all the voltage and current sources are replaced by their internal resistances.




let  $V_1$  and  $V_2$  be the unknown node voltage.

using KCL at Node 1:  $\frac{V_1}{(1\Omega)} + \frac{V_1 - V_2}{(5\Omega)} + 2 = 0 \Rightarrow 6V_1 - V_2 = -10$  (1)

using KCL at Node 2:  $\frac{V_2}{(2\Omega)} + \frac{V_2 - V_1}{(5\Omega)} - 5 = 0 \Rightarrow -2V_1 + 7V_2 = 50$  (2)

Solving eq's (1) + (2), we have  $V_1 = -0.5$  volts  $V_2 = 7$  volts

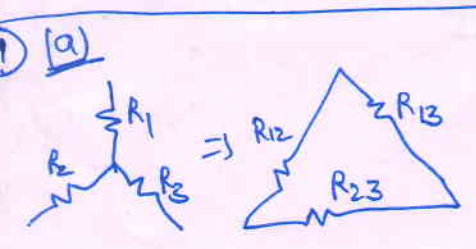Hence current:  $I = \frac{V_2 - V_1}{5} = \frac{7.5}{5} \Rightarrow I = 1.5$  Amperes




using the conversion formulae from  $Y \rightarrow \Delta$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$


For the given figure

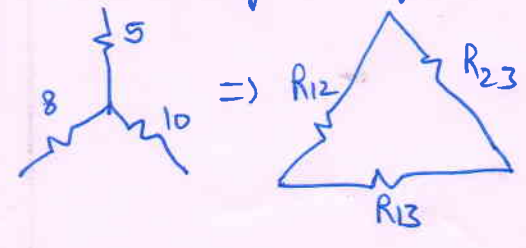

$$R_{12} = 8 + 5 + \frac{8 \times 5}{10} \Rightarrow R_{12} = 17 \Omega$$

$$R_{23} = 5 + 10 + \frac{5 \times 10}{8} \Rightarrow R_{23} = 21.25 \Omega$$
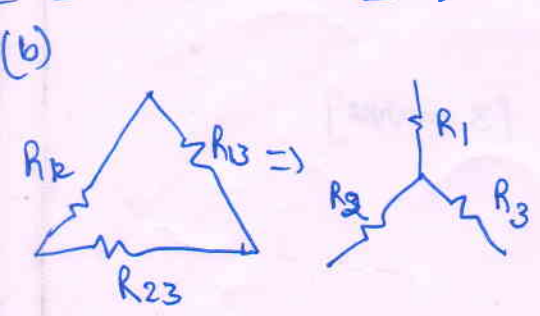
$$R_{13} = 8 + 10 + \frac{8 \times 10}{5} \Rightarrow R_{13} = 34 \Omega$$




using the conversion formulae for  $\Delta \rightarrow Y$

$$R_1 = \frac{R_{12} R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{13}}$$

$$R_3 = \frac{R_{13} R_{23}}{R_{12} + R_{23} + R_{13}}$$

For the given figure

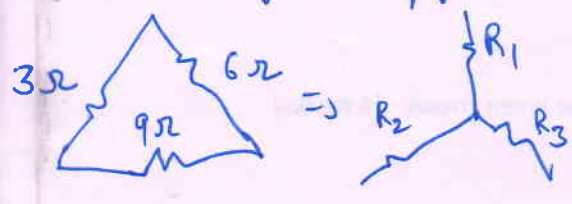


$$R_1 = \frac{6 \times 3}{18} \Rightarrow R_1 = 1 \Omega$$

$$R_2 = \frac{9 \times 3}{18} = R_2 = 1.5 \Omega$$

$$R_3 = \frac{6 \times 9}{18} = R_3 = 3 \Omega$$

(10)

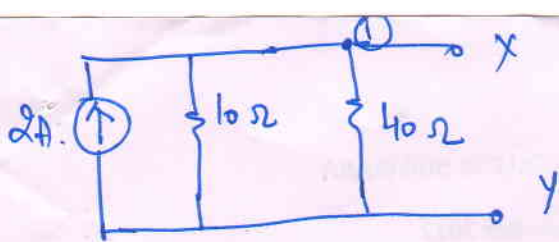


(i) Thevenin voltage  
using KCL at node ①

$$\frac{V_m}{40} + \frac{V_m}{10} - 2 = 0$$

$$\frac{V_m + 4V_m}{40} = 2$$

$$5V_m = 80 \Rightarrow V_m = 16 \text{ volts}$$

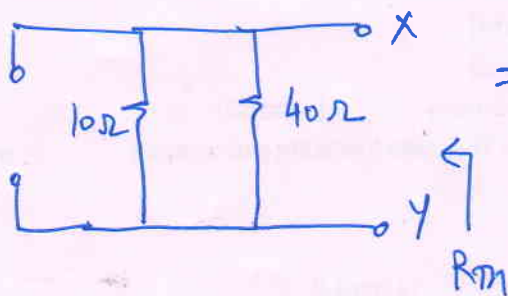(ii) Thevenin Resistance  
equivalent circuit can be drawn as:



$$\Rightarrow \frac{1}{R_m} = \frac{1}{40} + \frac{1}{10}$$

$$\Rightarrow R_m = 8 \Omega$$

484

(P.D. Vpadhyay)