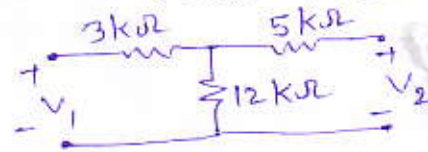


Q.1 Find the Laplace transform of $e^{-at} \sin bt$?

Q.2 Draw the Pole-zero diagram - $f(s) = \frac{s(s+1)}{s^2+2s+2}$

Q.3 Convert Z-Parameter into H-Parameter & find the Z-Parameter of the circuit ?



1.) Find the Laplace transform of $e^{-at} \sin bt$.

$\Rightarrow f(t) = e^{-at} \sin bt$

We know that $L[f(t)] = \int_0^{\infty} f(t) e^{-st} dt$

$\therefore L[f(t)] = \int_0^{\infty} e^{-at} e^{-st} \sin bt dt$ ~~let~~

Let, $I = \int_0^{\infty} e^{-(s+a)t} \sin bt dt$ --- (i)

\therefore we know $\int I \cdot II dt = I \int II dt - \int \left\{ \frac{dI}{dt} \int II dt \right\} dt$

$\therefore I = \sin bt \int_0^{\infty} e^{-(s+a)t} dt - \int_0^{\infty} \frac{d}{dt} \sin bt \int e^{-(s+a)t} dt dt$

$= \left[\frac{\sin bt \cdot e^{-(s+a)t}}{-(s+a)} \right]_0^{\infty} + \frac{b}{s+a} \int_0^{\infty} \cos bt \cdot e^{-(s+a)t} dt$

$= 0 + \frac{b}{s+a} \left[\cos bt \int_0^{\infty} e^{-(s+a)t} dt - \int_0^{\infty} \frac{d}{dt} \cos bt \int e^{-(s+a)t} dt dt \right]$

$= \frac{b}{s+a} \left[\frac{\cos bt \cdot e^{-(s+a)t}}{-(s+a)} \right]_0^{\infty} - \frac{b}{s+a} \int_0^{\infty} \sin bt e^{-(s+a)t} dt$

$I = \frac{b}{s+a} \left[\frac{1}{-(s+a)} - \frac{b}{s+a} I \right]$

$I \left[1 + \frac{b^2}{(s+a)^2} \right] = \frac{b}{(s+a)^2}$

$I = \frac{b}{(s+a)^2 + b^2}$


Ans. 2 $F(s) = \frac{s(s+1)}{s^2+2s+2}$

Zero $\rightarrow s = 0, -1$

Pole $\rightarrow s = \frac{-2 \pm \sqrt{4-8}}{2}$

$s = \frac{-2 \pm \sqrt{-4}}{2}$

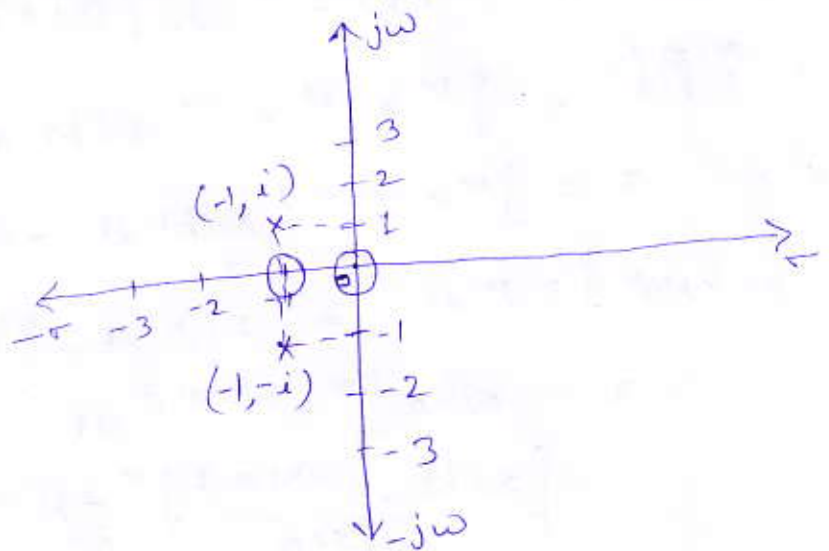$s = \frac{-2 \pm 2j}{2} \Rightarrow s = -1 + j, -1 - j$



Ans. 3 Z-Parameter ~

$V_1 = Z_{11} I_1 + Z_{12} I_2$ --- (1)

$V_2 = Z_{21} I_1 + Z_{22} I_2$ --- (2)

H-Parameter ! ~

$V_1 = H_{11} I_1 + H_{12} V_2$ --- (3)

$I_2 = H_{21} I_1 + H_{22} V_2$ --- (4)

from eq. (2)


$I_2 = -\left(\frac{Z_{21}}{Z_{22}}\right) I_1 + \frac{V_2}{Z_{22}}$ --- (5)

Put the value of ' I_2 ' from eq. (5) in eq. (1).

$$V_1 = Z_{11} I_1 + Z_{12} \left[-\left(\frac{Z_{21}}{Z_{22}}\right) I_1 + \frac{V_2}{Z_{22}} \right]$$

$$V_1 = I_1 \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right] + \frac{Z_{12}}{Z_{22}} V_2$$
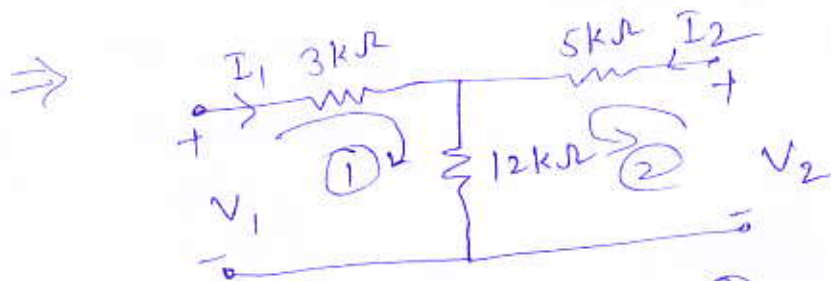
$$I_2 = -\left(\frac{Z_{21}}{Z_{22}}\right) I_1 + \frac{V_2}{Z_{22}}$$



Apply KVL at loop (1).

$$V_1 = 3 \times 10^3 I_1 + 12 \times 10^3 (I_1 + I_2)$$

$$V_1 = 15 \times 10^3 I_1 + 12 \times 10^3 I_2 \quad \text{--- (1)}$$

Apply KVL at loop (2).

$$V_2 = 5 \times 10^3 I_2 + 12 \times 10^3 (I_1 + I_2)$$

$$V_2 = 12 \times 10^3 I_1 + 17 \times 10^3 I_2 \quad \text{--- (2)}$$

from eq. (1) & (2), Z-Parameter will be -

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 15 \times 10^3 & 12 \times 10^3 \\ 12 \times 10^3 & 17 \times 10^3 \end{bmatrix} \Omega \quad \text{Ans.}$$